

INTRODUCTION TO ELECTRONICS

FINAL EXAM

1. In figure 1, T_1 - T_2 are identical and $\beta_F = h_{FE} = h_{fe} = 250$, $|V_{BE}| = 0.6$ V, $V_T = 26$ mV is given.
 - a) Calculate $R_1 = R_2$ and R_6 so that $R_i = 125$ k Ω and $V_i = 0$ when $V_o = 0$ (Assume $R_6 \gg r_{e2}$). **(12.5 p)**
 - b) Calculate the gain $K_V = v_o/v_i$ and the CMRR for the differential amplifier. **(12.5 p)**
2. In figure 2, for the BJT; $\beta_F = h_{FE} = h_{fe} = 100$, $V_{BE} = 0.6$ V, $V_A \rightarrow \infty$, $V_T = 26$ mV, for the MOSFET; $\beta_n = k_n = \mu_n C_{ox} \cdot (W/L) = 4$ mA/V², $V_{TH} = 1$ V, $\lambda = 0$ is assumed.
 - a) Calculate R_C , R_E , R_S so that the operation point of the BJT is $I_C = 2$ mA, $V_C = 6$ V, and $I_D = 2$ mA for the MOSFET. **(12.5 p)**
 - b) Calculate the input resistance R_i and the voltage gain v_o/v_g . **(12.5 p)**

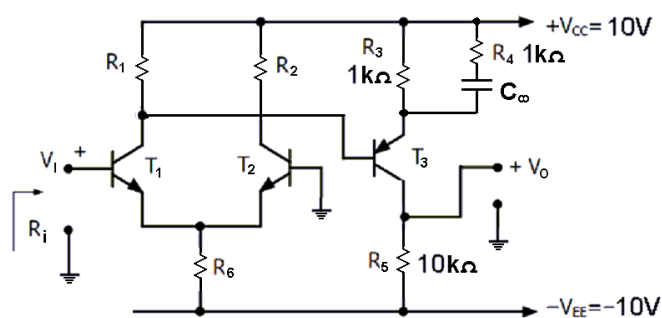


Figure 1

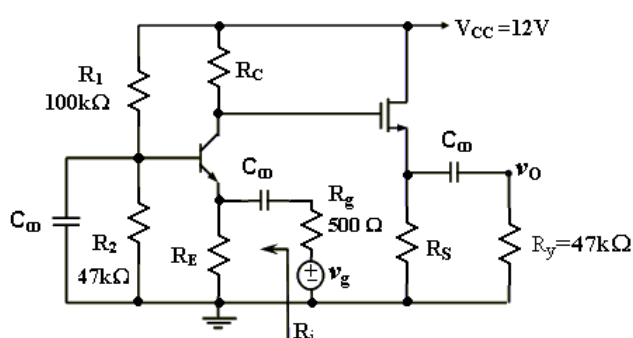


Figure 2

3. In figure 3, the operational amplifier is assumed ideal and the operational amplifier output voltage saturates at $V_{O+} = 5$ V and $V_{O-} = -5$ V. $V_{TH} = 1$ V, $\beta_n = k_n = \mu_n C_{ox} \cdot (W/L) = 500$ μ A/V² and $\lambda = 0$ is given for the MOSFET.
 - a) Express the voltage v_o in terms of v_{I1} , v_{I2} , i_D and the resistors. **(12.5 p)**
 - b) Assuming $R_1 = R_2 = R_F = 1$ k Ω , find the voltage v_o for the following conditions: **(12.5 p)**
 - i) $v_{I1} = 1.5$ V, $v_{I2} = 1$ V, $v_{I3} = 0.5$ V
 - ii) $v_{I1} = 0.5$ V, $v_{I2} = 3.5$ V, $v_{I3} = 2$ V
 - iii) $v_{I1} = -1$ V, $v_{I2} = 1.5$ V, $v_{I3} = 2.5$ V
4. In figure 4, assume the constant voltage drop model ($V_D = 0.7$ V) for the diodes.
 - a) Calculate I_{D1} and V_O for $R_1 = 5$ k Ω , $R_2 = 10$ k Ω . **(12.5 p)**
 - b) Calculate I_{D1} and V_O for $R_1 = 10$ k Ω , $R_2 = 5$ k Ω . **(12.5 p)**

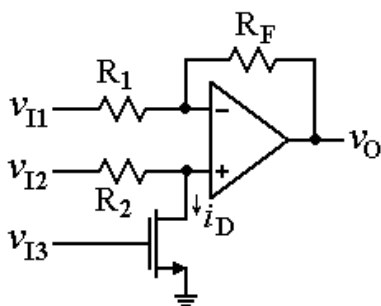


Figure 3

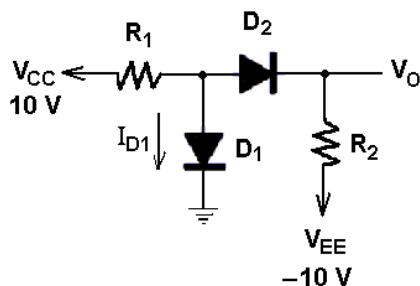


Figure 4