 




**ISTANBUL TECHNICAL  
UNIVERSITY**



**COMPUTER ENGINEERING**

**DIGITAL CIRCUITS LABORATORY  
EXPERIMENT REPORT**

**EXPERIMENT NO: 8**

**EXPERIMENT NAME: SEQUENTIAL CIRCUIT  
DESIGN**

**EXPERIMENT DATE : 19.04.2013**


**GROUP NO: 6**

**STUDENTS WHO DID THE EXPERIMENT:**

Student no	Name	Surname
040100113	MUSTAFA	UÇAR
040100117	TUĞRUL	YATAĞAN
040100124	EMRE	GÖKREM

**ASSISTANT NAME WHO ASSISTED THE  
EXPERIMENT: DENİZ DEMİRAY**

**1 )**

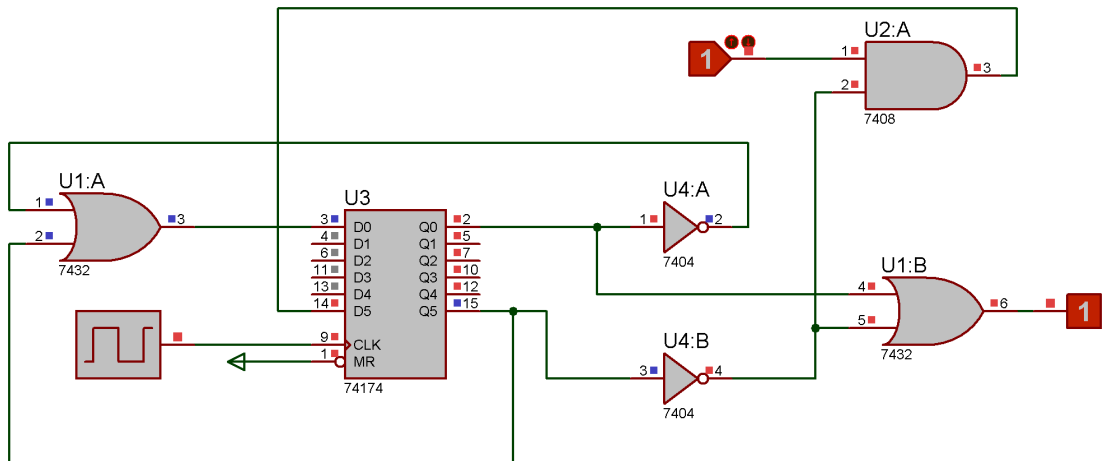


$$Q1^+ = Q1' + Q2$$


$$Q2^+ = X.Q2'$$

$$Z = Q1 + Q2'$$

<b>Q1<sup>+</sup>Q0<sup>+</sup>/Z</b>		
<b>Q1Q0\X</b>	<b>0</b>	<b>1</b>
<b>A – 00</b>	01,1	11,1
<b>B – 01</b>	00,0	10,0
<b>C – 11</b>	01,1	01,1
<b>D - 10</b>	01,1	01,1

**2)**

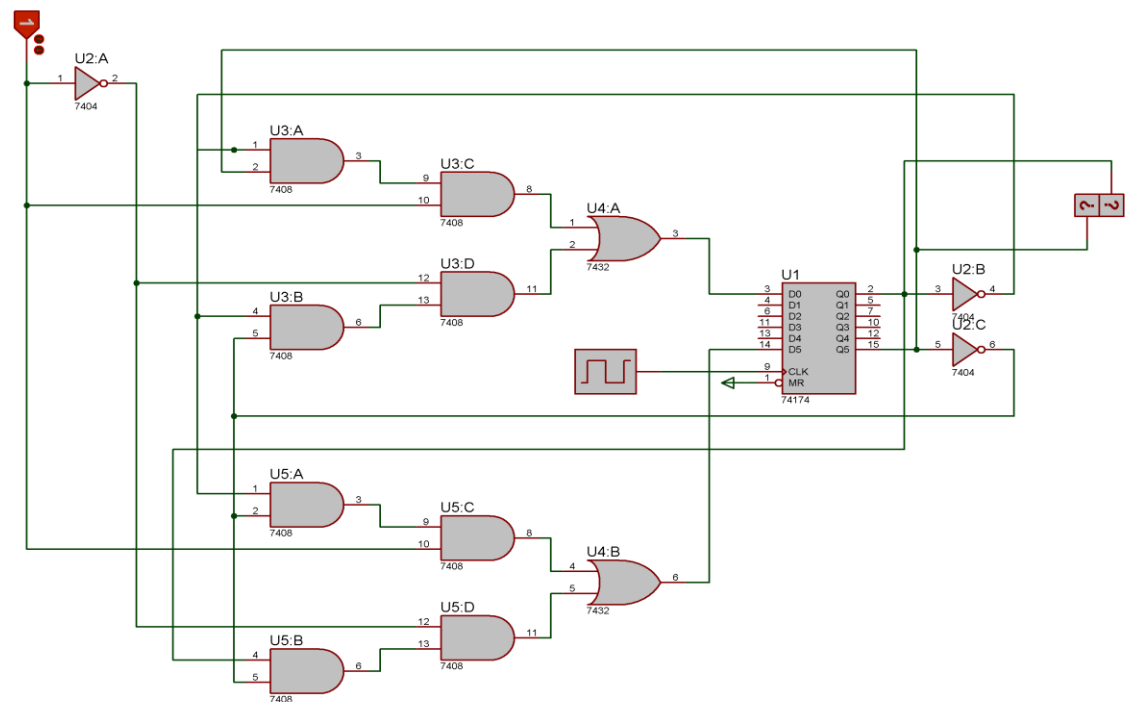

 

S'Z		
S\X	0	1
A	B	C
B	C	A
C	A	B

Q1 <sup>+</sup> Q0 <sup>+</sup>		
Q1Q0\X	0	1
00	01	10
01	10	00
10	00	01


D1		
Q1Q0\X	0	1
00	0	1
01	1	0
10	0	0

D0		
Q1Q0\X	0	1
00	1	0
01	0	0
10	0	1

$$D1 = X'Q0Q1' + XQ0'Q1' = Q1'(XQ0' + X'Q0)$$

$$D0 = X'Q0Q1' + XQ0'Q1 = Q0'(XQ1 + X'Q1')$$

3)

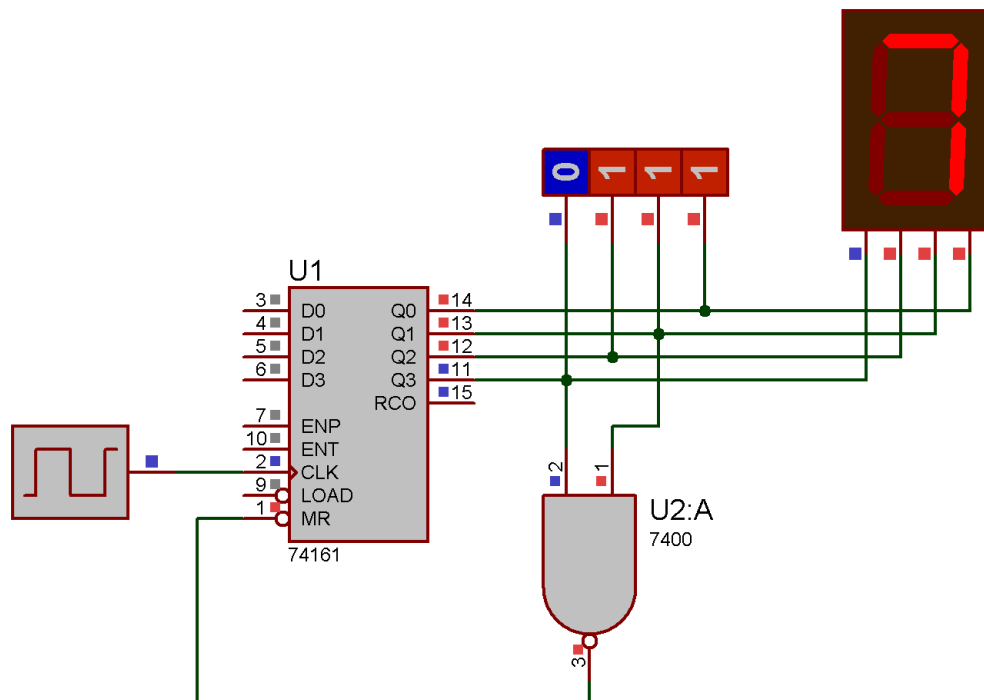

When 4<sup>th</sup> and 2<sup>nd</sup> bits are becomes 1, it means count is come to 1010. Because 1010 is smallest number that 4<sup>th</sup> and 2<sup>nd</sup> bits are 1. If both of them are 1, NAND gate will reset the counter.

4)

