

BLG222E - Computer Organization

Assignment 1

Design a 4-bit ripple counter using T flip flops in logism software. The counter should have one control input (X). If $X = 0$ the counter should count up (increment), and if $X = 1$ the counter should count down (decrement).

Save your design file in .circ format and upload it to ninova before its deadline.

