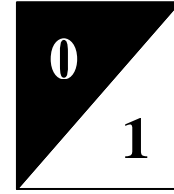




**ISTANBUL TECHNICAL  
UNIVERSITY**



**COMPUTER ENGINEERING**

**DIGITAL CIRCUITS LABORATORY  
EXPERIMENT REPORT**

**EXPERIMENT NO: 3**

**EXPERIMENT NAME: BINARY NUMBERS AND  
ARITHMETIC OPERATIONS**

**EXPERIMENT DATE : 15.03.2013**

**GROUP NO: 6**

**STUDENTS WHO DID THE EXPERIMENT:**

| Student no | Name    | Surname |
|------------|---------|---------|
| 040100113  | MUSTAFA | UÇAR    |
| 040100117  | TUĞRUL  | YATAĞAN |
| 040100124  | EMRE    | GÖKREM  |


**ASSISTANT NAME WHO ASSISTED THE  
EXPERIMENT: CUMALI TÜRKMENOĞLU**

**Aim:** Goal of this experiment is doing addition and subtraction operations on signed and unsigned numbers on digital circuits. Also some operations are tried on an ALU.

## Experiment #1

Truth table of a half adder is shown blow. All values are obtained from experiment.


| A | B | C | S |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

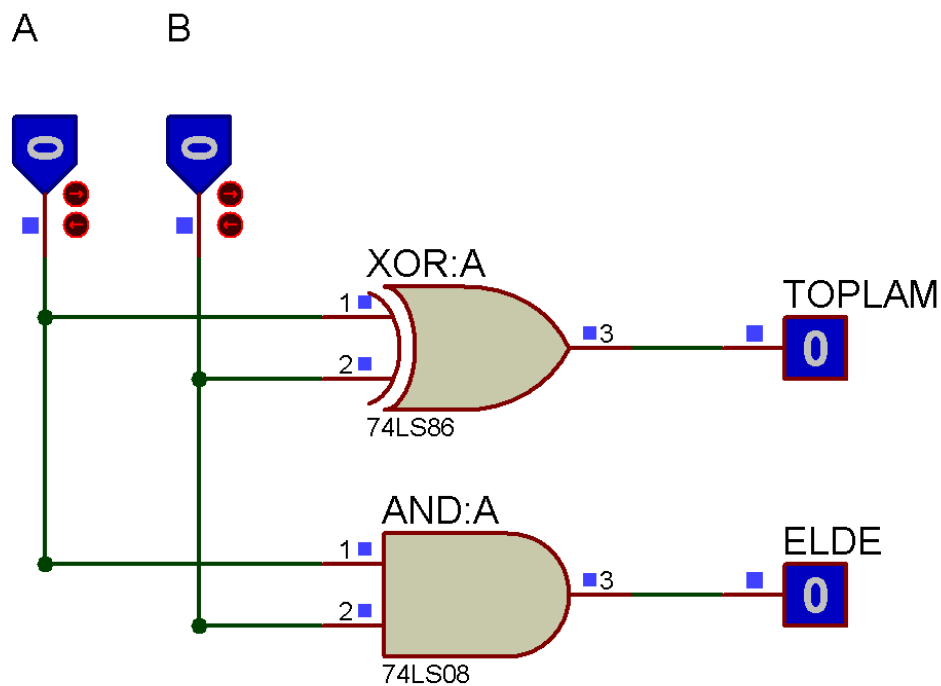

## Experiment #2

Truth table of a full adder is shown blow. All values are obtained from experiment.

| A | B | C <sub>i</sub> | C <sub>o</sub> | S |
|---|---|----------------|----------------|---|
| 0 | 0 | 0              | 0              | 0 |
| 0 | 0 | 1              | 0              | 1 |
| 0 | 1 | 0              | 0              | 1 |
| 0 | 1 | 1              | 1              | 0 |
| 1 | 0 | 0              | 0              | 1 |
| 1 | 0 | 1              | 1              | 0 |
| 1 | 1 | 0              | 1              | 0 |
| 1 | 1 | 1              | 1              | 1 |

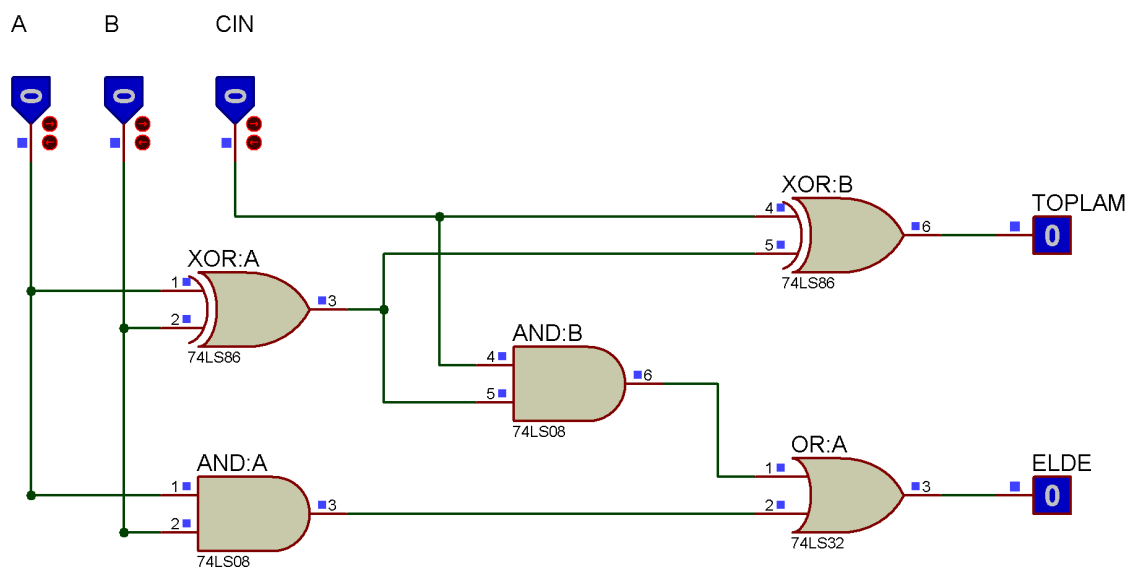


### Experiment #3

Expected results on addition and subtraction operations in 4-bit circuit are shown in table blow. All results obtained from experiment.

| ADDITION   |            |          |               |                |
|------------|------------|----------|---------------|----------------|
| UNSIGNED A | UNSIGNED B | CARRY    | BINARY RESULT | DECIMAL RESULT |
| 0101       | 0111       | 0        | 1100          | 12             |
| 1101       | 1001       | 1        | 0110          | 22             |
| 1111       | 1111       | 1        | 1110          | 30             |
| 0110       | 1101       | 1        | 0011          | 19             |
| SIGNED A   | SIGNED B   | OVERFLOW | BINARY RESULT | DECIMAL RESULT |
| 0101       | 0111       | 1        | 1100          | 12             |
| 1101       | 1001       | 1        | 0110          | 6              |
| 1111       | 1111       | 0        | 1110          | 2              |
| 0110       | 1101       | 0        | 0001          | 1              |


| SUBTRACTION |            |         |               |                |
|-------------|------------|---------|---------------|----------------|
| UNSIGNED A  | UNSIGNED B | BORROW  | BINARY RESULT | DECIMAL RESULT |
| 0101        | 0111       | 1       | 1110          | 14             |
| 1101        | 1001       | 0       | 0100          | 4              |
| 1111        | 1111       | 0       | 0000          | 0              |
| 0110        | 1101       | 1       | 1001          | 9              |
| SIGNED A    | SIGNED B   | OVEFLOW | BINARY RESULT | DECIMAL RESULT |
| 0101        | 0111       | 0       | 1110          | -2             |
| 1101        | 1001       | 1       | 0100          | 4              |
| 1111        | 1111       | 0       | 0000          | 0              |
| 0110        | 1101       | 0       | 1001          | -7             |

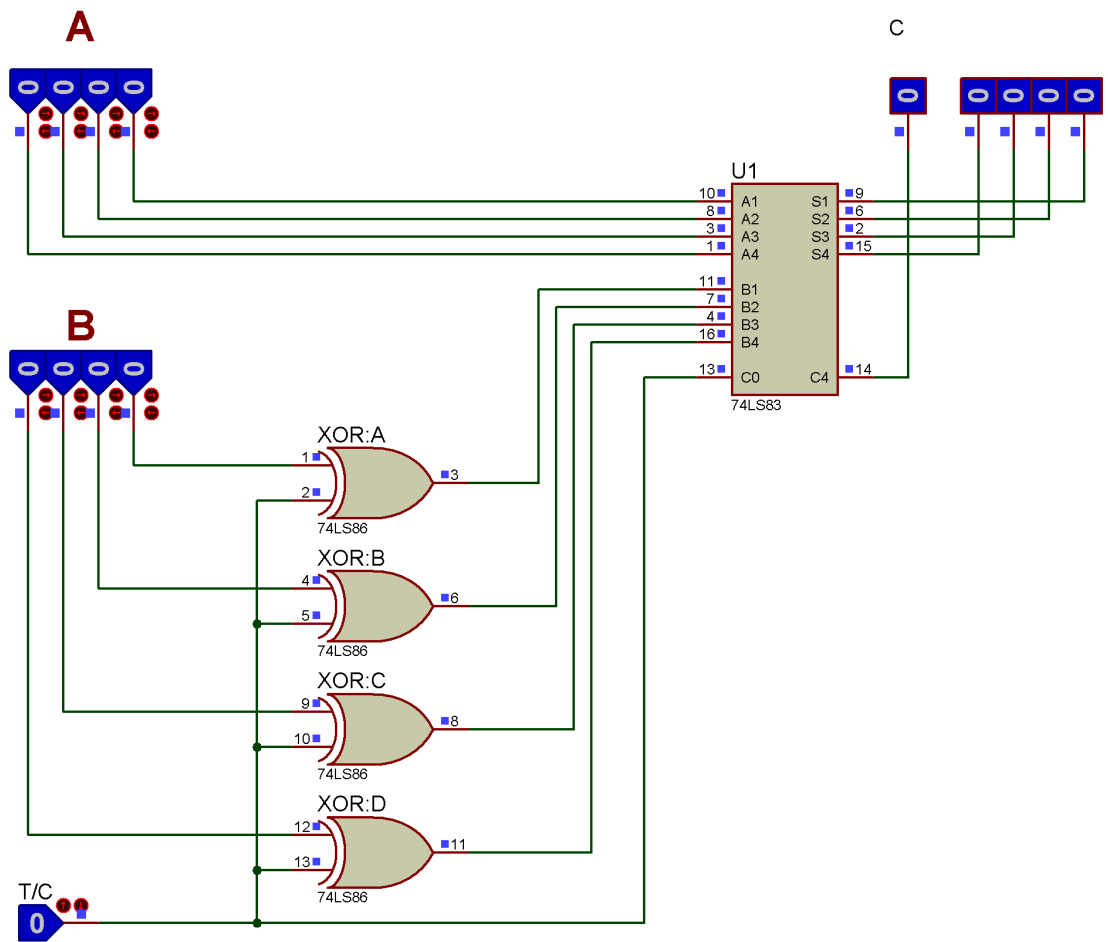

## Experiment #4

DM74LS1814-Bit Arithmetic Logic Unit Function Table

| Mode Select Inputs |    |    |    | Active HIGH Operands & F <sub>n</sub> Outputs |                                |
|--------------------|----|----|----|---|--------------------------------|
|                    |    |    |    | Logic   | Arithmetic                     |
| S3                 | S2 | S1 | S0 | (M = H)                                       | (M = L) (C <sub>n</sub> = H)   |
| L                  | L  | L  | L  | $\bar{A}$                                     | A                              |
| L                  | L  | L  | H  | $\bar{A} + \bar{B}$                           | A + B                          |
| L                  | L  | H  | L  | $\bar{A} B$                                   | A + $\bar{B}$                  |
| L                  | L  | H  | H  | Logic 0                                       | minus 1                        |
| L                  | H  | L  | L  | $\bar{A} \bar{B}$                             | A plus $\bar{A} \bar{B}$       |
| L                  | H  | L  | H  | $\bar{B}$                                     | (A + B) plus $\bar{A} \bar{B}$ |
| L                  | H  | H  | L  | $A \oplus B$                                  | A minus B minus 1              |
| L                  | H  | H  | H  | $\bar{A} \bar{B}$                             | AB minus 1                     |
| H                  | L  | L  | L  | $\bar{A} + B$                                 | A plus AB                      |
| H                  | L  | L  | H  | $\bar{A} \oplus \bar{B}$                      | A plus B                       |
| H                  | L  | H  | L  | B   | (A + $\bar{B}$ ) plus AB       |
| H                  | L  | H  | H  | AB  | AB minus 1                     |
| H                  | H  | L  | L  | Logic 1                                       | A plus A (Note 1)              |
| H                  | H  | L  | H  | $A + \bar{B}$                                 | (A + B) plus A                 |
| H                  | H  | H  | L  | A + B   | (A + $\bar{B}$ ) plus A        |
| H                  | H  | H  | H  | A   | A minus 1                      |

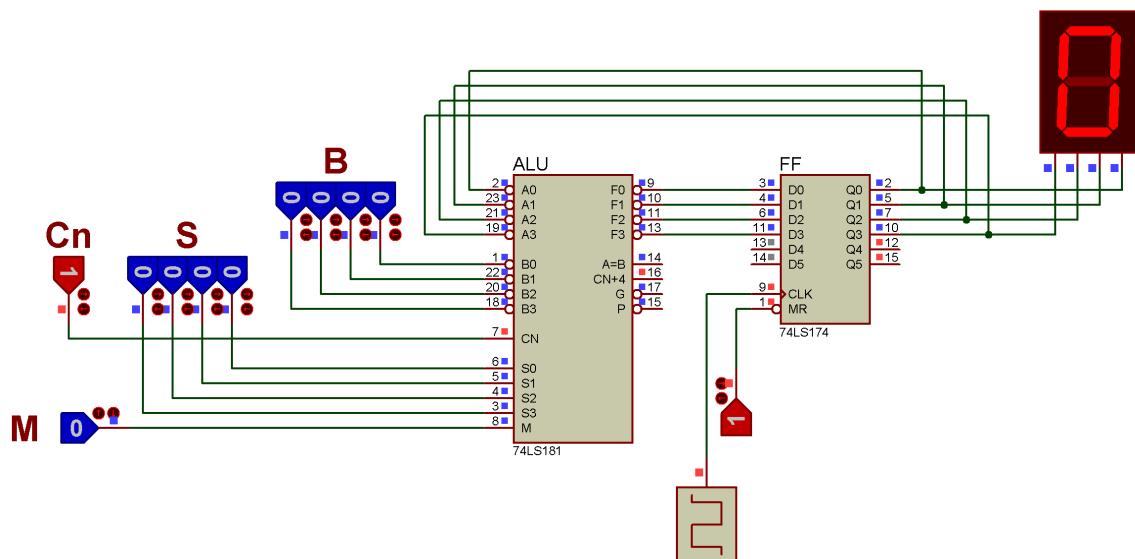

### Answer of Question #3

