

# INTRODUCTION to ELECTRONICS and ANALOG ELECTRONICS CIRCUITS LABORATORY



## EXPERIMENT REPORT

<b>Experiment Name</b>	Linear Applications of Operational Amplifiers
<b>Lab Assistant</b>	Berat DOĞAN
<b>Author of the Report (Name / No / Department)</b>	Tuğrul YATAĞAN 040100117 Computer Engineering
<b>Group Number and Experiment Date</b>	D27 15.11.2013

<b>Report Score</b>	<b>Deliver Date</b>	<b>Receive Date</b>
	22.11.2013	


# INTRODUCTION to ELECTRONICS and ANALOG ELECTRONICS CIRCUITS LABORATORY

## Aim of the Experiment

In this experiment session, we investigate basic understanding of operational amplifiers (op-amps) for performing linear applications such as inverting amplifiers, non-inverting amplifiers and some mathematical functions.
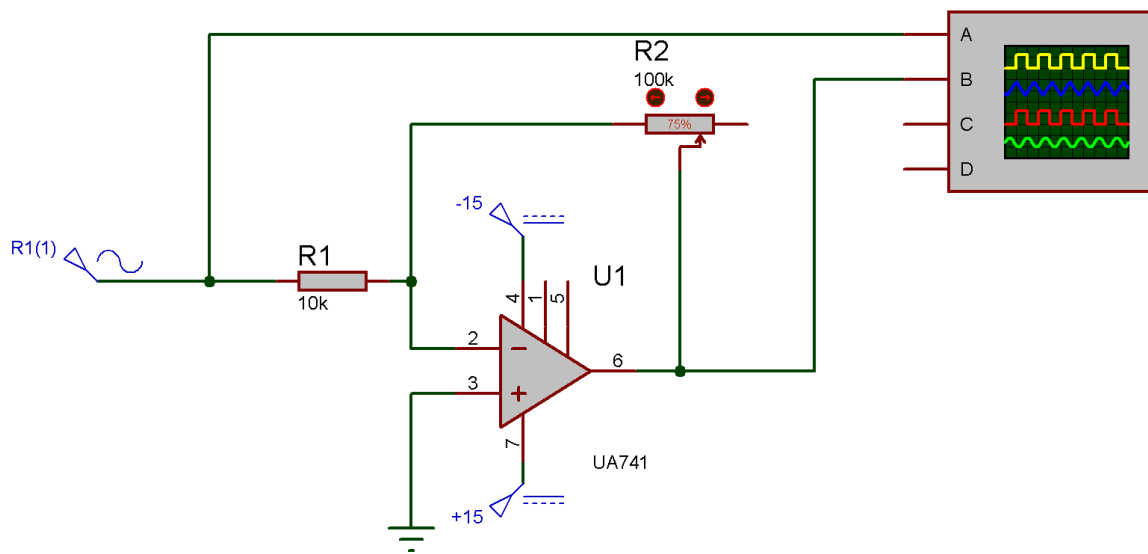
## Exp #1 Inverting OP-AMP

We provide 2V peak to peak sinusoidal wave signal to input. R1 is 10k  $\Omega$  resistor and R2 is a 100k  $\Omega$  linear potentiometer. Since R2 is potentiometer, we can set various values for R2 and measure the peak to peak voltage of output signal from oscilloscope.




$$V_{in} = 2V (V_{pp})$$

$R_2(\Omega)$	Measured $V_{out} (V_{pp})$	Theoretical $V_{out} (V_{pp})$
100k	18.4 V	20 V
75k	14.4 V	15 V
50k	9.46 V	10 V
25k	2.54 V	5 V
10k	2 V	2 V

Theoretical  $V_{out}$  calculated from the voltage gain equation of the inverting amplifier circuit is:

$$\frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1}$$

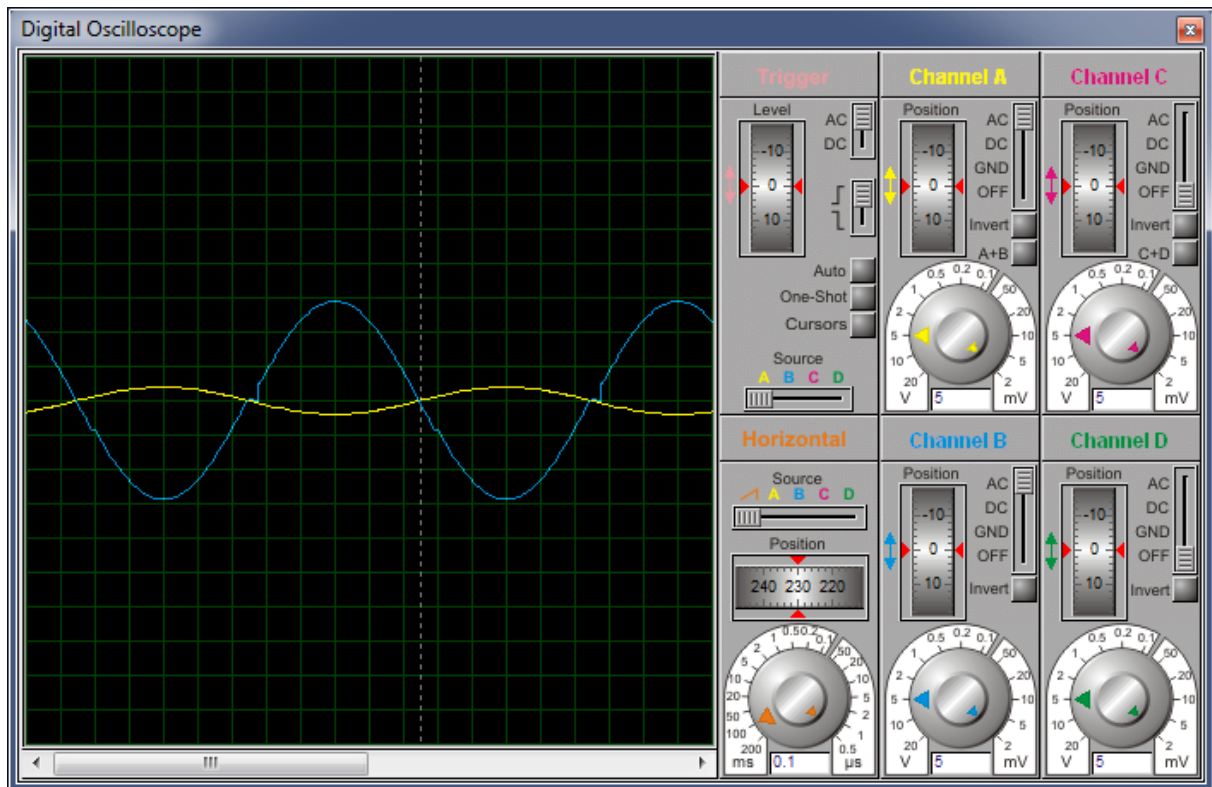
# INTRODUCTION to ELECTRONICS and ANALOG ELECTRONICS CIRCUITS LABORATORY



As can be seen in simulation oscilloscope screen, input signal (yellow line) is amplified and inverted to output signal (blue line).
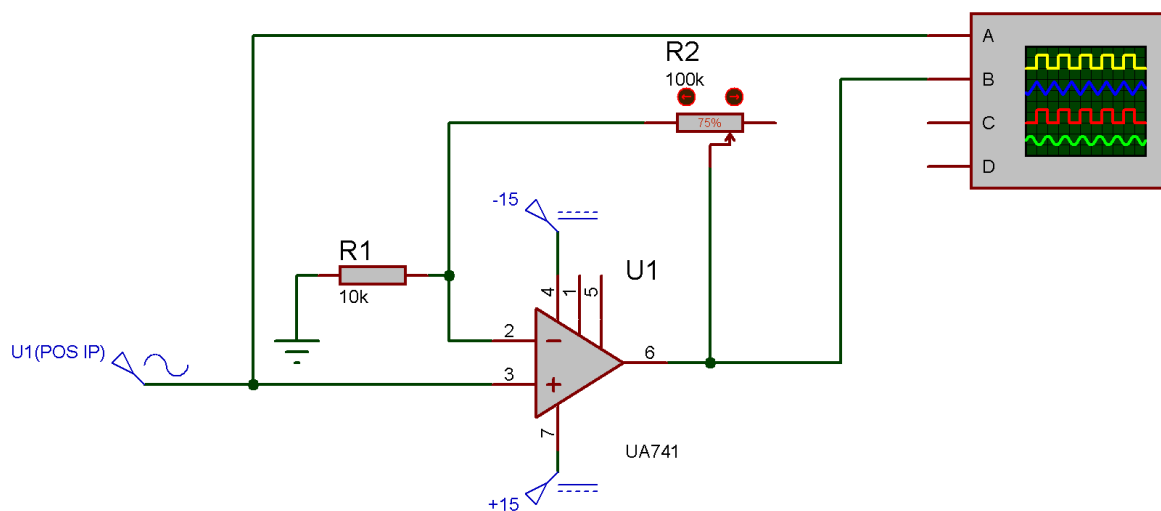
## Exp #2 Non-Inverting OP-AMP

We provide 2V peak to peak sinusoidal wave signal to input like first experiment. R1 is 10k  $\Omega$  resistor and R2 is a 100k  $\Omega$  linear potentiometer. Since R2 is potentiometer, we can set various values for R2 and measure the peak to peak voltage of output signal from oscilloscope.




# INTRODUCTION to ELECTRONICS and ANALOG ELECTRONICS CIRCUITS LABORATORY

$$V_{in} = 2V (V_{pp})$$

$R_2(\Omega)$	Measured $V_{out} (V_{pp})$	Theoretical $V_{out} (V_{pp})$
100k	20.2 V	22 V
75k	16.6 V	17 V
50k	11.9 V	12 V
25k	6.91 V	7 V
10k	3.95 V	4 V

Theoretical  $V_{out}$  calculated from the voltage gain equation of the non-inverting amplifier circuit is:
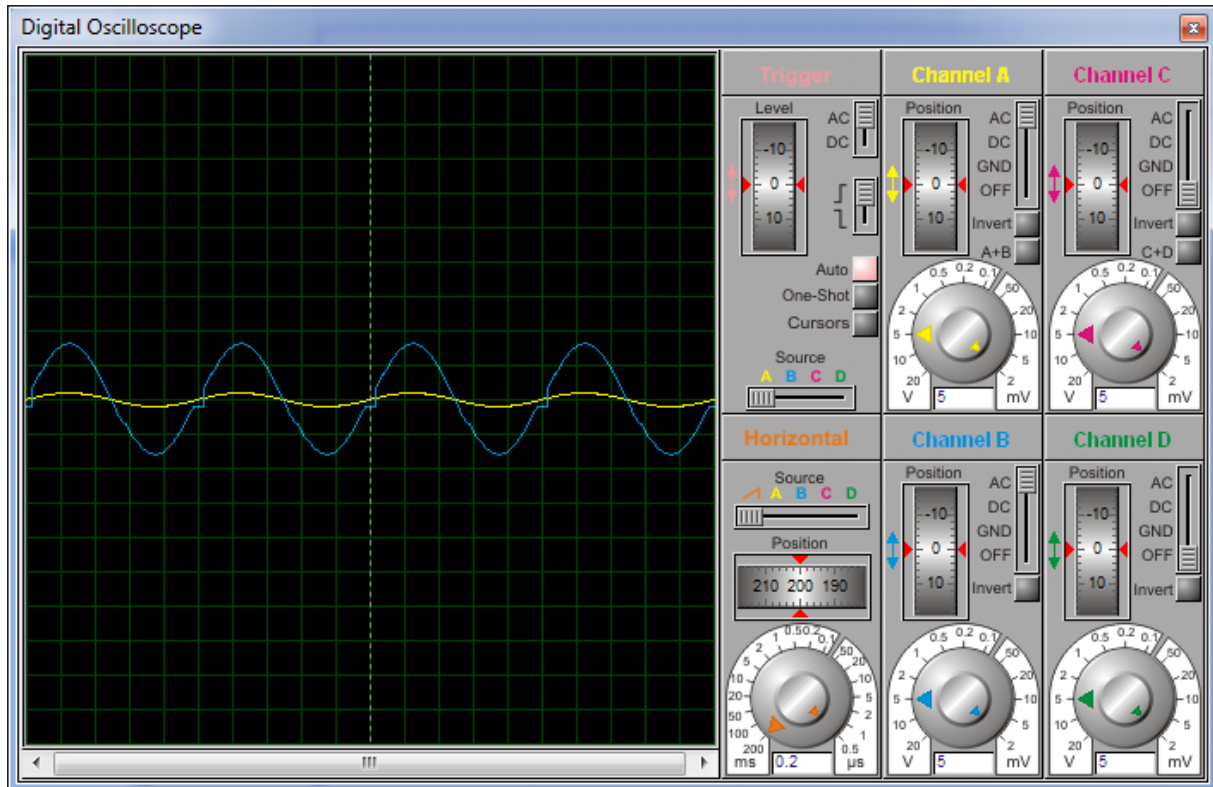
$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$



As can be seen in simulation oscilloscope screen, input signal (yellow line) is amplified and to output signal (blue line).

## Exp #3 Summing Amplifier

We provide 5V DC signal as  $V_1$  and 6V peak to peak sinusoidal wave signal as  $V_2$  to input.  $R_1$  is 8.2k $\Omega$  resistor,  $R_2$  is 2.7k $\Omega$  resistor and  $R_3$  is 8.2k $\Omega$  resistor for adjusting  $a = 1$  and  $b = 3$  in output equation;

$$V_o = -(aV_1 + bV_2) \text{ so;}$$



$$V_o = -(V_1 + 3V_2)$$

# INTRODUCTION to ELECTRONICS and ANALOG ELECTRONICS CIRCUITS LABORATORY

Which is actually; the voltage gain equation of the summing amplifier:

$$V_o = -\left(\frac{R_3}{R_1} V_1 + \frac{R_3}{R_2} V_2\right)$$

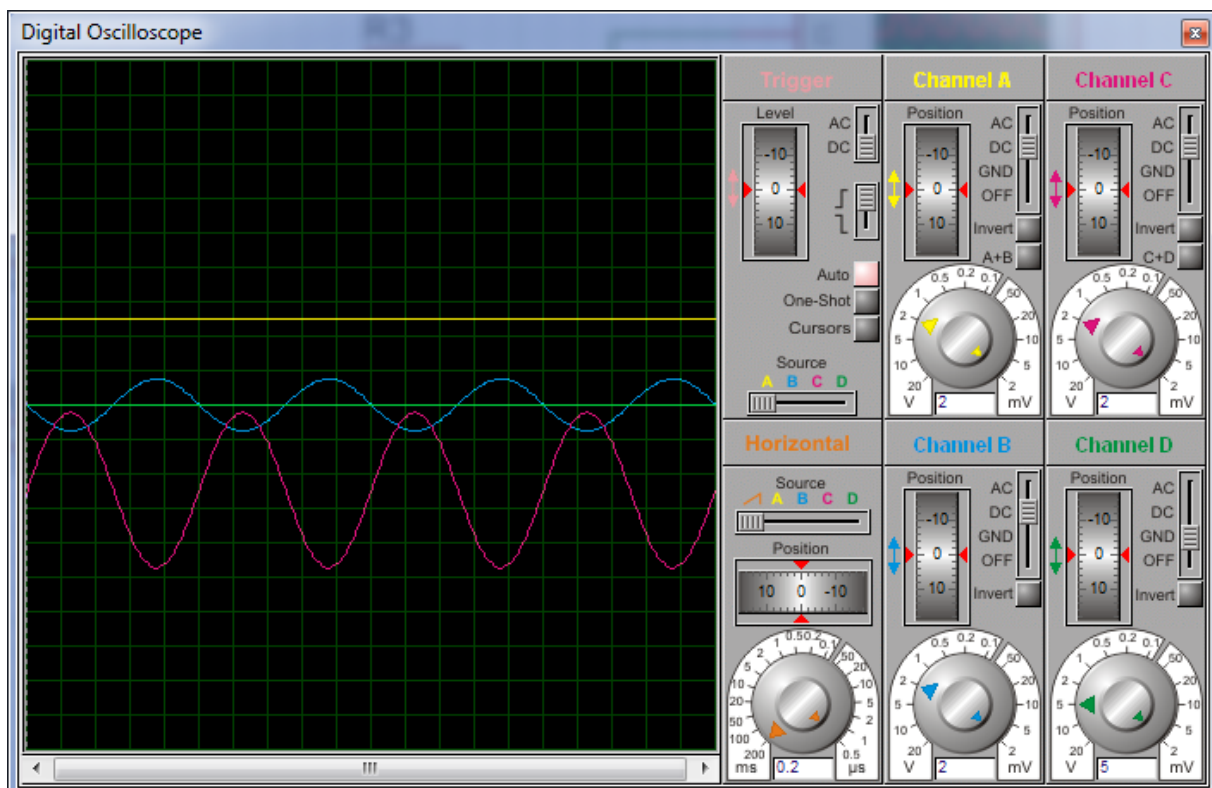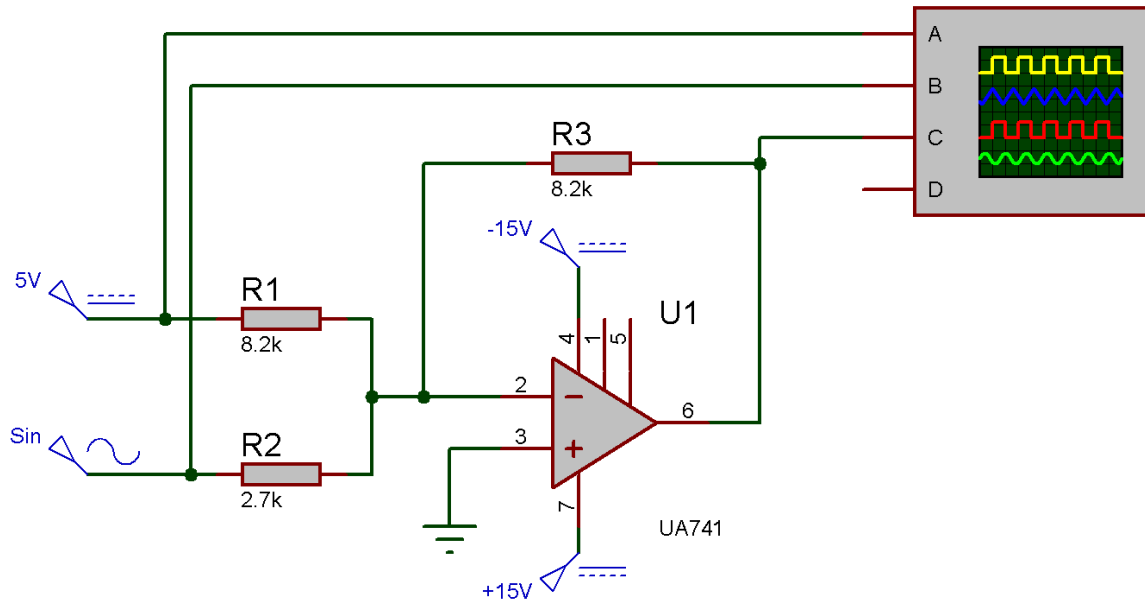Then we measure the peak to peak voltage of output signal from oscilloscope.





As can be seen in simulation oscilloscope screen; input signal 5V DC as  $V_1$  (yellow line), input signal 6V sinusoidal as  $V_2$  (blue line), ground (green line) and the output signal (purple line). Output is like inverted and amplified sinusoidal wave with 5V offset below the ground.

# INTRODUCTION to ELECTRONICS and ANALOG ELECTRONICS CIRCUITS LABORATORY
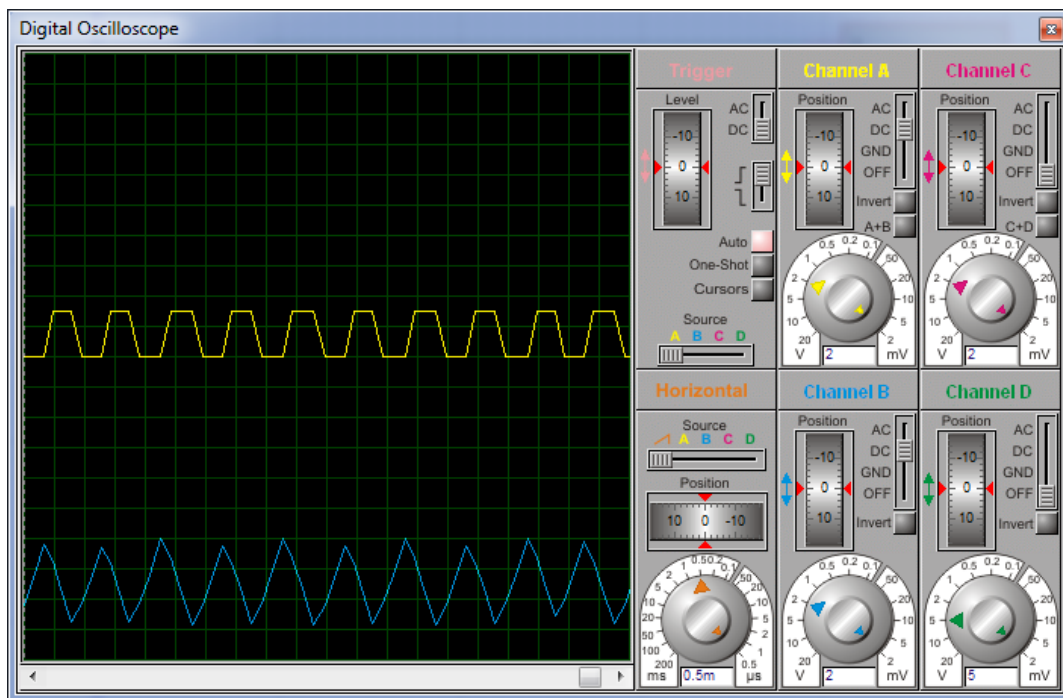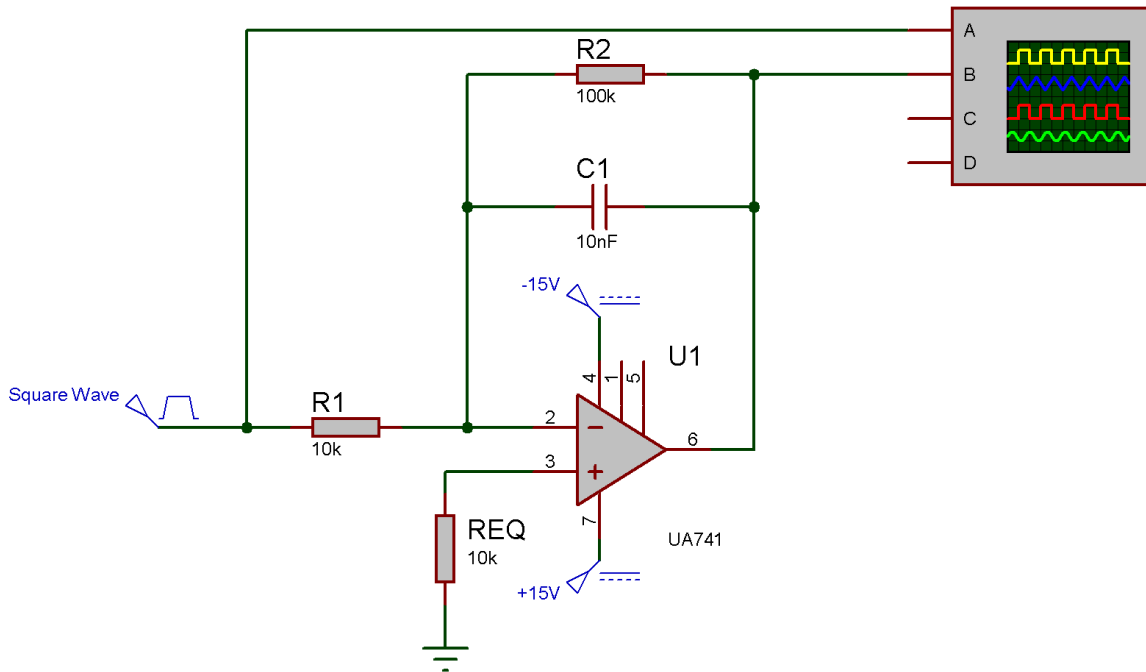
## Exp #4 OP-AMP Integrator

We provide 5V peak to peak square wave signal as  $V_{in}$ , R1 is 10k $\Omega$  resistor, R2 is 100k $\Omega$  resistor and  $R_{eq}$  is 10k $\Omega$  resistor for adjusting voltage equation of the op-amp integrator.

$$V_o = -\frac{1}{RC} \int V_1 dt + V_{o(t=0)}$$



As can be seen in simulation oscilloscope screen; input signal 5V square wave as  $V_{in}$  (yellow line) and the output signal (blue line). Output is integral form of input signal, so integral form of square wave signal is rectangle wave signal.