
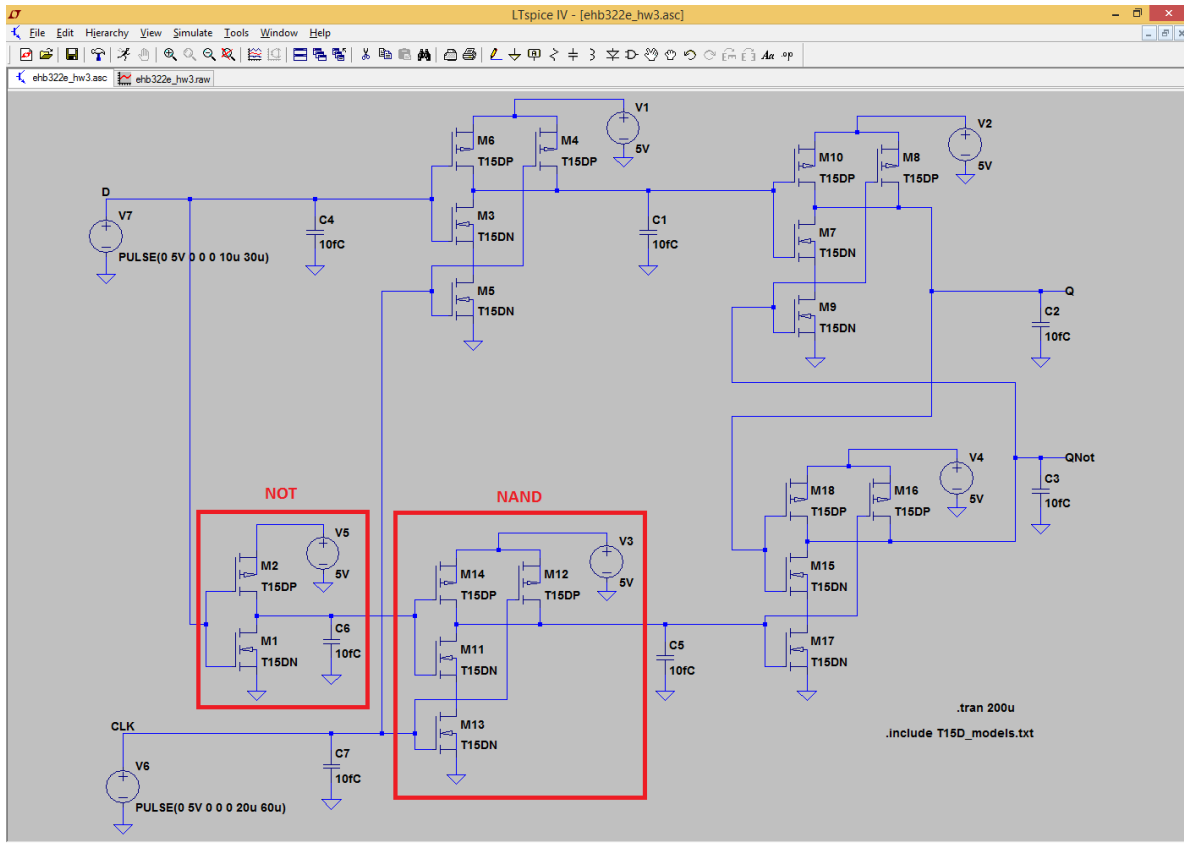


# CMOS D-flip-flop

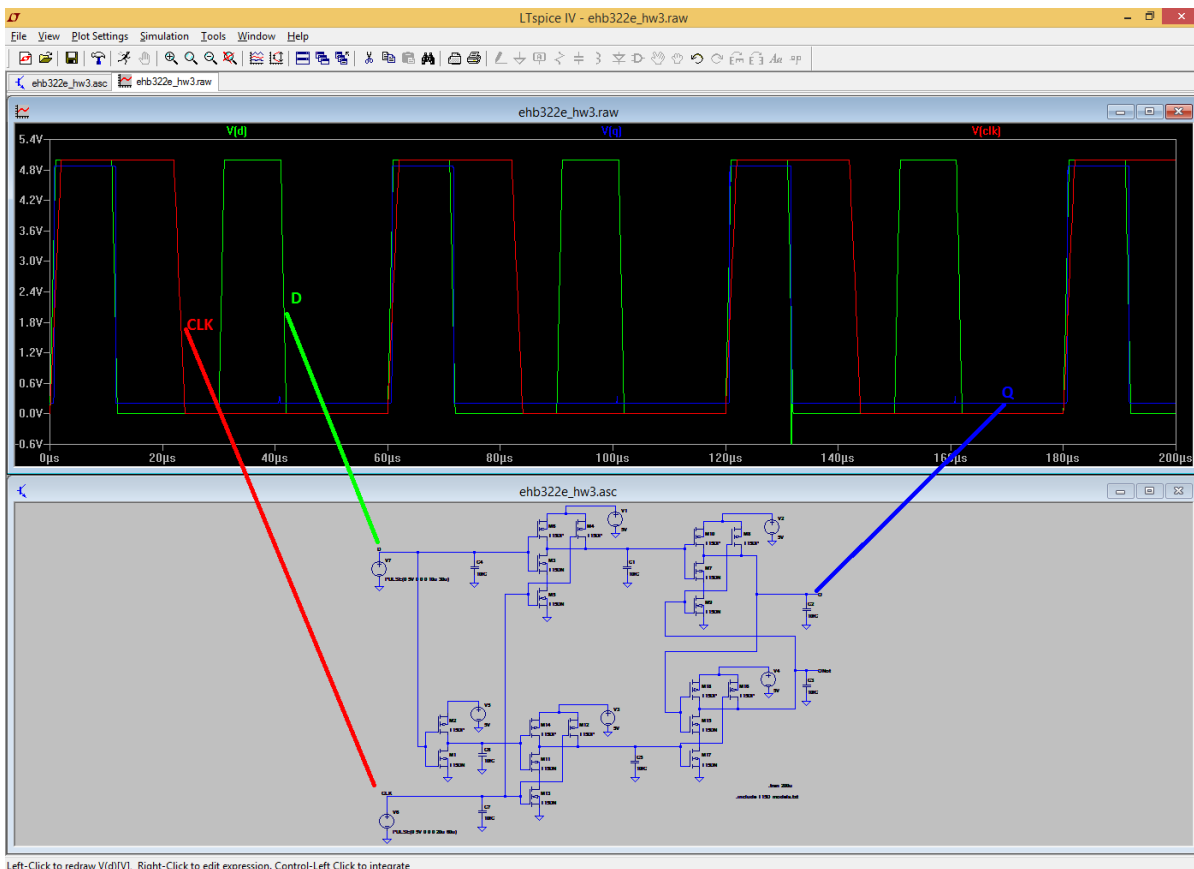


## Q output with D and CLK



## W.C. PD at Q with D input


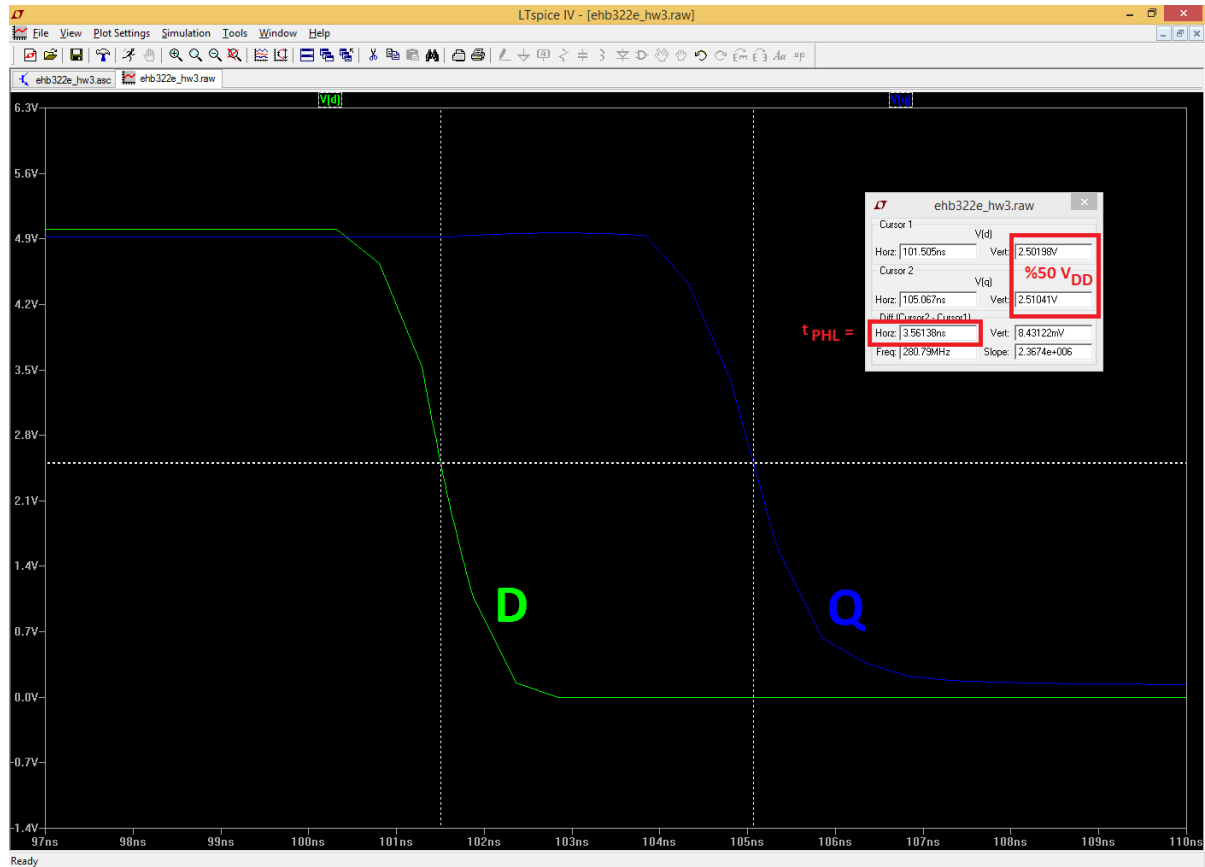
## W.C. Total $t_{PHL}$ at Q with D input



## W.C. Total $t_{PLH}$ at Q with D input

