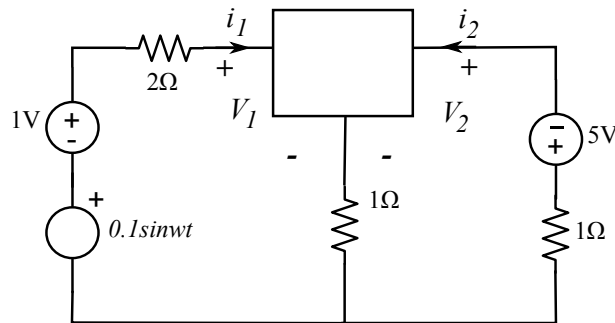


(Due : 24/12/2012)

1. Nonlinear 3-terminal element is defined by $V_1 = i_1$, $V_2 = V_1^2 + i_2$ and $i_1 > 0$. (a) Determine the operating point of the 3-terminal element. (b) Draw linear small signal equivalent circuit using only 2-terminal circuit elements. (c) Find the approximate solution of $i_2(t)$.




2. .

- 4.77** Find the Thévenin equivalent with respect to the terminals a,b in the circuit in Fig. P4.77.

PSPICE

Figure P4.77

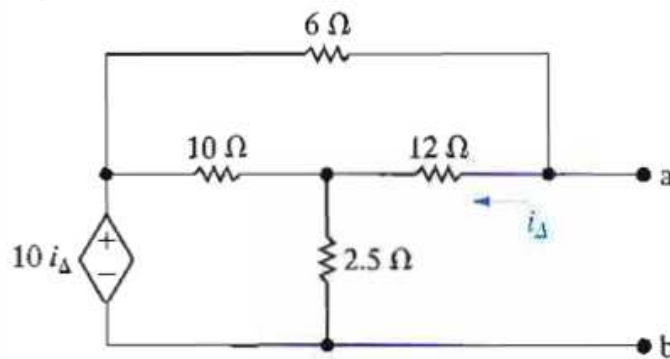


3. .

- 4.93** Use the principle of superposition to find the current i_o in the circuit in Fig. P4.93.

PSPICE

Figure P4.93

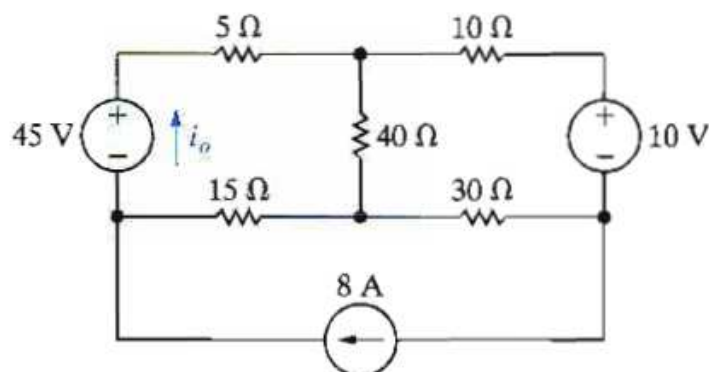

4. .

4.72 Find the Thévenin equivalent with respect to the terminals a,b for the circuit seen in Fig. P4.72.

PSPICE

Figure P4.72

