

**QUESTION 3: [30 Points]**

Assume that the ALU (Adder and Logic Unit) in Figure 3 has only the following features:

**Feature 1:** ALU can perform the following logical operations:

*AND* (  $AC \leftarrow AC \wedge M[AR]$  )

*XOR* (  $AC \leftarrow AC \oplus DR$  ).

**Feature 2:** ALU cannot perform the subtraction directly. However, it can perform complement and add operations to perform subtraction.

Considering the basic computer in Figure 3 with the ALU defined above, write the sequence of register transfer statements needed to execute the commands in the table below.

**HINT-1:** Fetch and Decode is already done in T0, T1, T2, and T3 cycles.

**HINT-2:** Addressing mode bit (IR[15]) is already checked.

**HINT-3:** EA is the effective address in the AR at the time where the commands start executing.

| <i>Symbol</i> | <i>Opcode</i> | <i>Symbolic Representation</i>                  | <i>Description</i>                 |
|---------------|---------------|---|------------------------------------|
| XOR           | 000           | $AC \leftarrow AC \oplus M[EA]$                 | XOR with AC                        |
| SUB           | 001           | $AC \leftarrow AC - M[EA]$                      | Subtract memory from AC            |
| EXC           | 010           | $AC \leftarrow M[EA],$<br>$M[EA] \leftarrow AC$ | Exchange AC and memory             |
| BPA           | 011           | If (AC > 0)<br>Then (PC ← EA)                   | Branch if AC positive and non-zero |

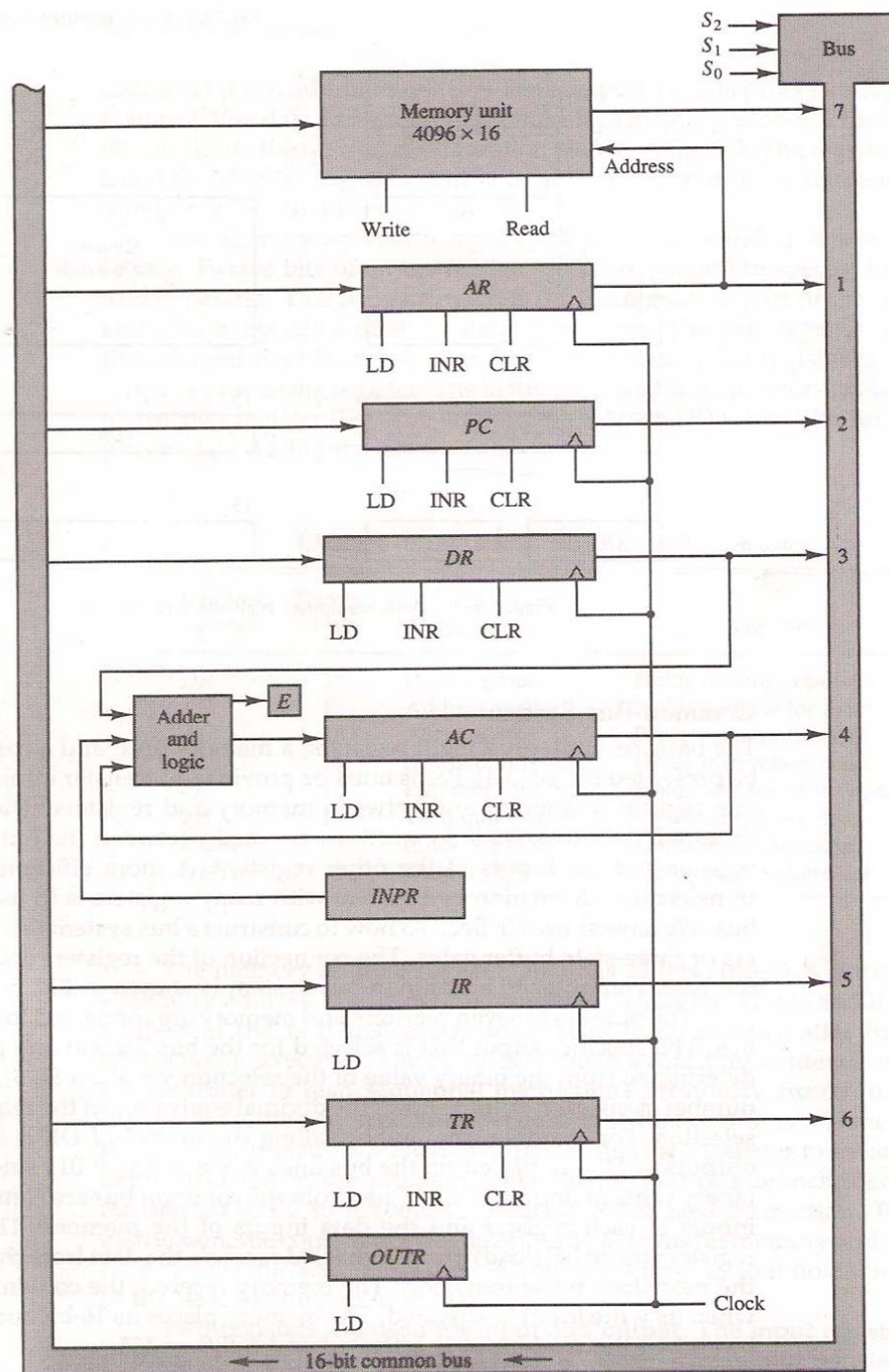


Figure 5-4 Basic computer registers connected to a common bus.

XOR:

D0T4:  $DR \leftarrow M[AR]$

D0T5:  $AC \leftarrow AC \oplus DR, \quad SC \leftarrow 0$

SUB:

D1T4:  $DR \leftarrow M[AR]$

D1T5:  $DR \leftarrow AC, AC \leftarrow DR,$

D1T6:  $AC \leftarrow AC'$

D1T7:  $AC \leftarrow AC + 1$

D1T8:  $AC \leftarrow AC + DR, \quad SC \leftarrow 0$

EXC

D2T4:  $DR \leftarrow M[AR]$

D2T5:  $M[AR] \leftarrow AC, AC \leftarrow DR, \quad SC \leftarrow 0$

BPA

D3T4: if( $AC=0$  AND  $AC(15)=0$ )

Then

$PC \leftarrow AR, SC \leftarrow 0$