

# BLG311E Formal Languages and Automata

## Finite State Machines

A.Emre Harmanci    Osman Kaan Erol    Tolga Ovatman

2012

## Outline

- 1 Definitions and Models (Mealy and Moore)
- 2 Sequential System Design using Algorithmic State Machines
- 3 State Equivalence, State Compatibility and State Reduction
  - State Equivalence and Reduction of Completely Specified State Tables
  - State Compatibility, Compatibility Relation and Reduction of Incomplete

## Computing Machines

### Computer

A computer is a general purpose *machine* which can be programmed to carry out a finite set of arithmetic or logical operations(*computation*).

## Computing Machines

### Machine

A machine is a tool consisting of one or more generally moving parts that is constructed to achieve a particular goal. However, the advent of electronics technology has led to the development of devices without moving parts that are considered machines.

## Computing Machines

### Abstract Machine

An abstract machine, is a theoretical model of a computer hardware or software system.

## Finite State Machine(FSM)

An FSM has a mathematical model defined by a quintuple  $(S, I, O, \delta, \omega)$ , where:

- $S$ : Set of states.
- $I$ : Input alphabet (a finite, non-empty set of symbols)
- $O$ : Output alphabet (a finite, non-empty set of symbols)
- $\delta$ : The transition function defined on  $I \times S \rightarrow S$
- $\omega$ : The output function defined on either  $S \rightarrow O$  or  $I \times S \rightarrow O$

## FSM properties

A finite state machine should hold the following properties

- 1 It has finite input and output alphabets
- 2 It is deterministic

### Deterministic Machine

For a deterministic machine the outcome of a transition from one state to another given a certain input can be predicted for every occurrence. In a deterministic finite state machine, for each pair of state and input symbol there is one and only one transition to a next state.

## FSM properties

A finite state machine should hold the following properties

- 3 It has transducer capability.

### Transducer

A transducer machine has two alphabets: an input alphabet and an output alphabet. Transducers are said to be able to *transform* inputs to output.

## Transducers

When realizing transducers with digital circuits the concept of discrete-time is used.

### Discrete Time

Discrete time is the discontinuity of a function's time domain that results from sampling a variable at a finite interval. One of the fundamental concepts behind discrete time is an implied (actual or hypothetical) system clock.

## Transducers

In sequential synchronous digital circuits both the input and output functions are determined by combinational circuits. On the other hand, in determining next state of the circuit the characteristic equation of the flip-flop becomes effective as well. In a formal way

$$S(r^+) = Q(S(r), \delta(S(r), I(r)))$$

- SR type:  $q^+ = S + R'q$
- D type:  $q^+ = D$
- JK type:  $q^+ = Jq' + K'q$
- T type:  $q^+ = T \oplus q$

For the case of a D flip-flop the next state is determined by

$$S(r^+) = \delta(S(r), I(r))$$

## Transducers

Transducers holds some certain properties in digital discrete-time systems.

- Sequence: Discretization is performed by the sequence order of the labels.  $n$  is the length of the sequence.
- $[\Lambda]$ : A singleton set which only includes an *empty string*.
- $I^*$ : Set of input sequences :  $I^* = [\Lambda] \cup I \cup I^2 \cup \dots \cup I^n \dots$
- $O^*$ : Set of output sequences :  $O^* = [\Lambda] \cup O \cup O^2 \cup \dots \cup O^n \dots$
- Suppose that the transducer performs  $w = f(x)$  transformation where  $w \in O$  and  $x \in I$ . Function  $f$  holds following properties:

- Length preservation:  $|w| = |x| = n; n \in \mathbb{N}$
- Prefix inclusivity:  
 $(x = x_1x_2) \wedge (w = w_1w_2) \wedge (|x_1| = |w_1|) \Rightarrow w_1 = f(x_1)$

## An example Machine

Suppose we want to design a machine that reads numerical codes input from a keypad and accepts *only one* certain key combination. For this particular case( $S, I, O, \delta, \omega$ ) can be defined as:

- $I \in \{0, 1, 2, \dots, 9\}$ .

We may want to restrict the number of digits to 4, for example  $1234 \in I^4$

- $S$ : At each keystroke we need to control if the correct digit is input. In our case  $|S| = 5$  or  $s_i \in S : 0 \leq i \leq 4$

- $O = \{open, closed\}$  is the output alphabet.

- Our machine is going to accept the code after 4 correct inputs. The final state  $F = s_4$ . Let's ignore any wrong combinations at this moment for the sake of simplicity


- Since we only have one correct combination  $\delta$  can be defined as follows  $\delta$  :

$$\begin{aligned} (s_0, 1) &\rightarrow s_1 \\ (s_1, 9) &\rightarrow s_2 \\ (s_2, 0) &\rightarrow s_3 \\ (s_3, 3) &\rightarrow s_4 \end{aligned}$$

- Our output function  $\omega$  maps  $s_i \rightarrow closed$  where  $0 < i \leq 3$  and  $s_4 \rightarrow open$
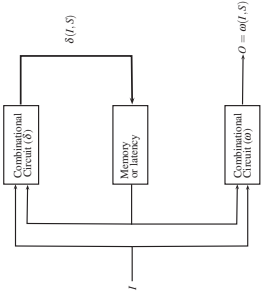
## Machine Types


A Mealy machine<sup>1</sup> is a finite-state machine whose output values are determined both by its current state and the current inputs  $I \times S \rightarrow O$ .



<sup>1</sup>The Mealy machine is named after George H. Mealy, who presented the concept in a 1955 paper, "A Method for Synthesizing Sequential Circuits"
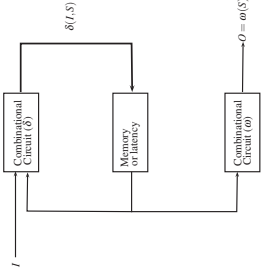
## Machine Types


A Moore machine<sup>2</sup> is a finite-state machine, whose output values are determined solely by its current state  $S \rightarrow O$ .



<sup>2</sup>The Moore machine is named after Edward F. Moore, who presented the concept in a 1955 paper, "Gedanken-experiments on Sequential Machines"
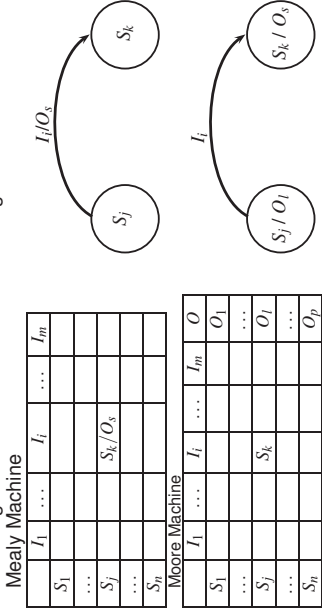
## Modeling FSMs

Following elements can be used in modeling FSMs:




## Example

A coffee vending machine that accepts coins of 5, 10 and 25 cents, gives coffee for 15 cents and returns the change. Let's build Mealy and Moore models of this machine.

Mealy model,  $S_i / i, j$ :  $x$  denotes money input so far,  $i$  change return and  $j$  holds  $C$  for coffee output and  $-$  for no output.

State diagram:

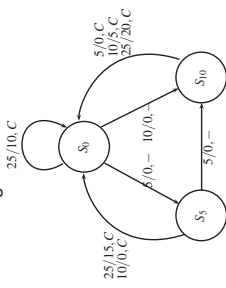

State table:

	5	10	25
$S_0$	$S_5/0,-$	$S_{10}/0,-$	$S_0/10,C$
$S_5$	$S_{10}/0,-$	$S_0/0,C$	$S_0/15,C$
$S_{10}$	$S_0/0,C$	$S_0/5,C$	$S_0/20,C$


## Example

For Moore model the number of states need to be at least the number of different State/output pairs in the Mealy model. States should not be assigned to the coins input. When no coins are input current state is preserved.

State table:


	5	10	25	Output
$S_0$	$S_5$	$S_{10}$	$S_{25}$	0,-
$S_5$	$S_{10}$	$S_{15}$	$S_{30}$	0,-
$S_{10}$	$S_{15}$	$S_{20}$	$S_{25}$	0,-
$S_{15}$	$S_5$	$S_{10}$	$S_{25}$	0,C
$S_{20}$	$S_5$	$S_{10}$	$S_{25}$	5,C
$S_{25}$	$S_5$	$S_{10}$	$S_{25}$	10,C
$S_{30}$	$S_5$	$S_{10}$	$S_{25}$	15,C
$S_{35}$	$S_5$	$S_{10}$	$S_{25}$	20,C

## Digital System Design

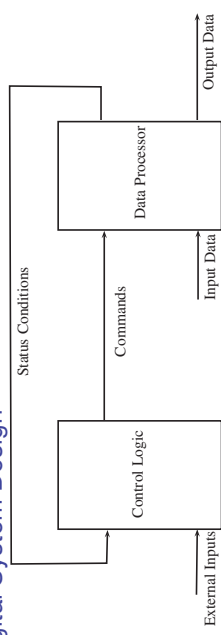

- When designing digital hardware, a general approach is to handle data processing and control operations separately.
- The control logic and data processing tasks of a digital system are specified by means of a hardware algorithm.
- One of the common ways in representing an algorithm is by using a flowchart.

## Algorithmic State Machines

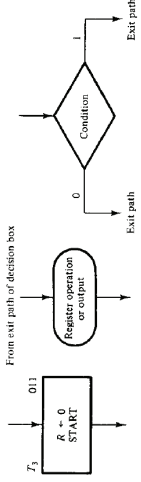


Algorithmic state machine(ASM) is a special type of flowchart that has been developed specifically to define digital hardware algorithms.


ASMs are composed of three basic elements:

- The state box: Denoted as a rectangle within which are written register operations or output signals.
- The decision box: Diamond shaped box describing the effect of an input on the control subsystem.
- The conditional box: Oval shaped box unique to ASMs. Register operations or outputs listed in the box are generated during a given state provided that the input condition is satisfied.

## An ASM and an equivalent Statechart

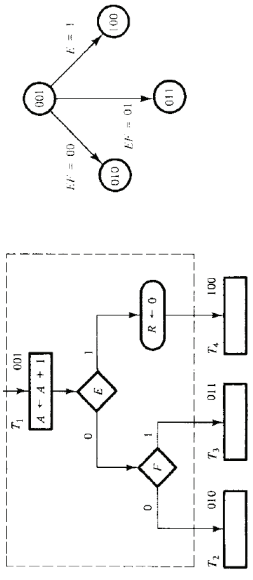

## Timing properties of ASMs

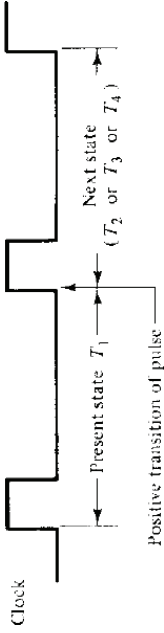


The major difference between an ASM and a flowchart is in interpreting its timing properties. In a flowchart every transition between elements is done sequentially while in an ASM operations in a block is done simultaneously. By the second rise of the clock signal's positive edge:

- 1 Register A is incremented
- 2 If E=1 register R is cleared
- 3 Depending on the values of E control is transferred to next state.


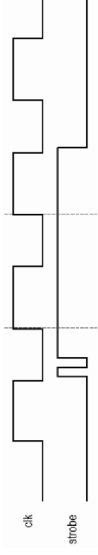
## Timing differences between Mealy and Moore Circuits

Let's investigate three different designs of a circuit to detect the rising edge of a slow "strobe" input and generate a "short" output pulse.<sup>3</sup>





<sup>3</sup>Examples taken from Dr. Pong P. Chu's book titled "RTL Hardware Design Using VHDL: Coding for Efficiency, Portability, and Scalability"


## A Moore Machine Design

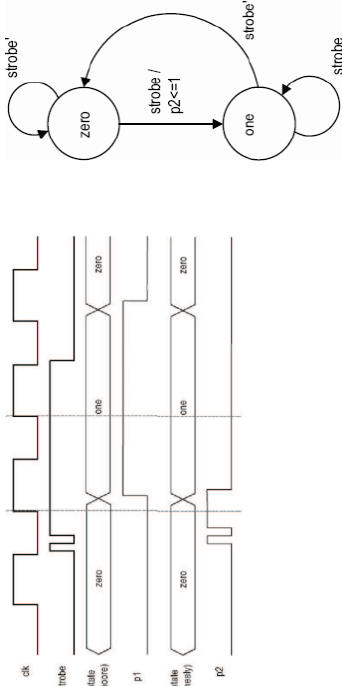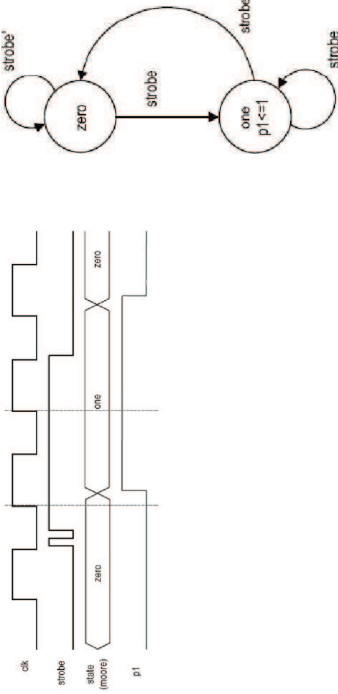

## A Mealy Machine Design

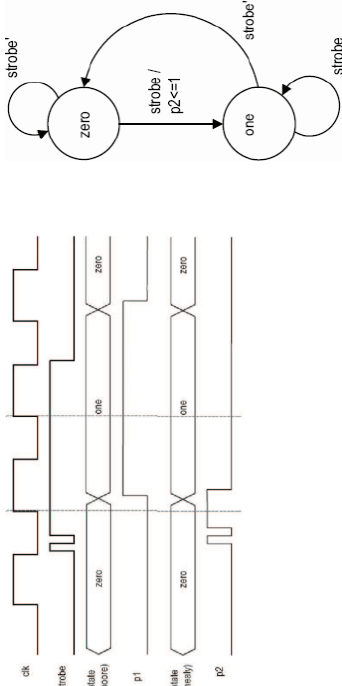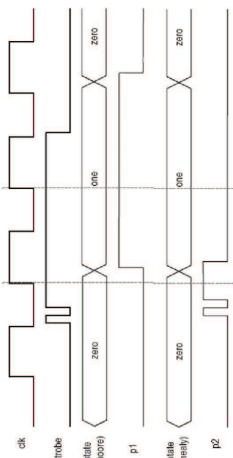

### Another Mealy Machine Design

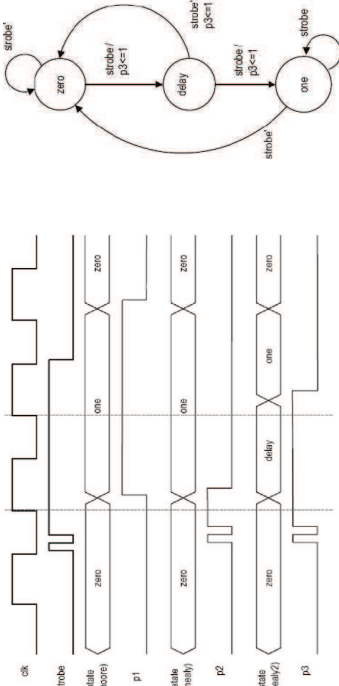


### Example


An ASM that calculates the largest of three positive integers is to be designed. Machine will kick off by an input signal switching to "1" and load the numbers successively to eight bit registers A, B and C. After the machine finishes its run and gets back to the starting state register "D" is going to hold the largest number  $D = Max(A, B, C)$ . A combinational subtraction circuit is going to be used for comparison operations. Subtraction result is going to be held in a separate "carry" flag.

- 1 Sketch the ASM diagram of the machine, defined above.
- 2 Design and sketch the controller unit assigning each state to a D flip-flop.
- 3 Design and sketch data unit. State the input signals of the units you have used.


### Example - ASM 1

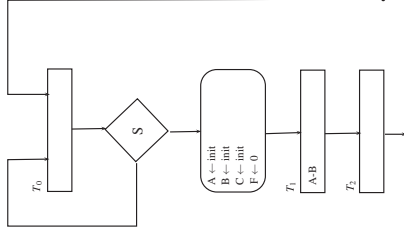


### Example - ASM 2

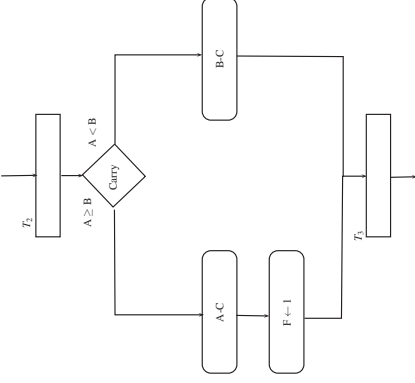

### Example - ASM 3

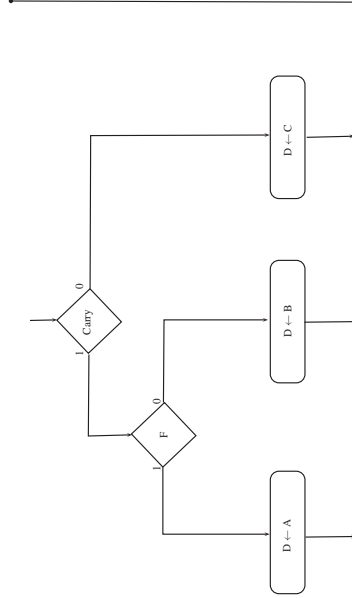


### Example - States

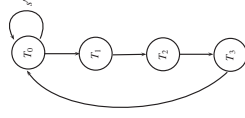

$$\begin{aligned} T_0 &= T_3 + s'T_0 \\ T_1 &= sT_0 \\ T_2 &= T_1 \\ T_3 &= T_2 \end{aligned}$$
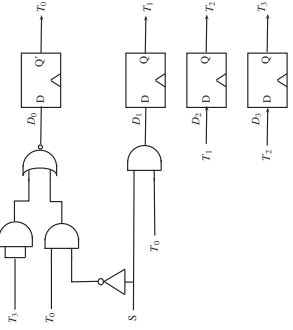
### Example - Control Unit


$$\begin{aligned} T_0 &= T_3 + s'T_0 \\ T_1 &= sT_0 \\ T_2 &= T_1 \\ T_3 &= T_2 \end{aligned}$$


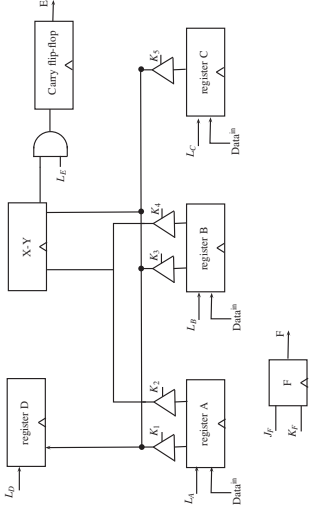
### Example - Data Unit


$$\begin{aligned} L_A &= L_B = L_C = sT_0 \\ L_D &= T_3 \\ L_E &= T_3 \\ J_F &= ET_2 \\ K_F &= sT_0 \end{aligned}$$

$$\begin{aligned} K_1 &= T_3FE \\ K_2 &= T_1 + T_2E \\ K_3 &= T_1 + T_3F'E \\ K_4 &= T_2E' \\ K_5 &= T_2 + T_3E' \end{aligned}$$


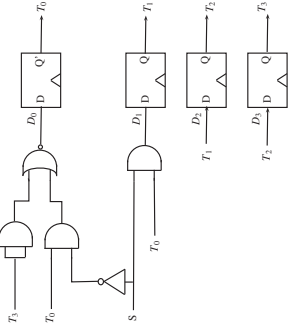
### Example - Control Unit

$$\begin{aligned} T_0 &= T_3 + s'T_0 \\ T_1 &= sT_0 \\ T_2 &= T_1 \\ T_3 &= T_2 \end{aligned}$$



### State equivalence

During a system's design iterations designers may come up with non-optimal state tables containing equivalent states. In order to overcome this situation mathematical definition of equivalency and state reduction principles are used.

#### Equivalence Relation

A given binary relation  $\sim$  on a set  $S$  is said to be an equivalence relation if and only if it is reflexive, symmetric and transitive.

Equivalently,  $\forall s_i, s_j, s_k \in S$ :

- $s_i \sim s_i$
- $s_i \sim s_j \Rightarrow s_j \sim s_i$
- $s_i \sim s_k \wedge s_k \sim s_j \Rightarrow s_i \sim s_j$

### State equivalence

Using the mathematical definition of equivalency the set of machine states can be partitioned into equivalence classes. Equivalence classes should include

- Explicitly equivalent states
- Implicitly equivalent states, whose equivalency depends on other states' equivalency.

#### State Equivalency Conditions

The necessary and sufficient conditions for two states in a state table to be equivalent are: For all the inputs of those states

- Outputs should be the same
- Successing conditions should
  - be explicitly or implicitly equivalent
  - not have any outputs that doesn't conform equivalency

Dependency identification of states can be performed using dependency tables and undirected relation graphs. Let's consider the following state table.

$S/I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_3/0$
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_3/0$
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$

We shall build a dependency table step by step based on the state dependencies.

$S/I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	$S_1/0$	$S_5/1$	$S_1/0$	
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_3/0$
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_3/0$
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$
$S_1$	$S_1$	$S_2$	$S_3$	$S_4$
$S_2$				
$S_3$				
$S_4$				
$S_5$				
$S_6$				
$S_7$				
$S_8$				

S/I	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	I <sub>4</sub>			
S <sub>1</sub>	S <sub>1</sub> /0	S <sub>2</sub> /1	S <sub>6</sub> /1	S <sub>1</sub> /0			
S <sub>2</sub>	S <sub>5</sub> /1	S <sub>5</sub> /0	S <sub>6</sub> /0	S <sub>5</sub> /0			
S <sub>3</sub>	S <sub>5</sub> /1	S <sub>7</sub> /0	S <sub>4</sub> /0	S <sub>3</sub> /0			
S <sub>4</sub>	S <sub>1</sub> /0	S <sub>7</sub> /1	S <sub>4</sub> /1	S <sub>3</sub> /0			
S <sub>5</sub>	S <sub>5</sub> /0	S <sub>6</sub> /1	S <sub>5</sub> /1	S <sub>5</sub> /0			
S <sub>6</sub>	S <sub>2</sub> /1	S <sub>6</sub> /0	S <sub>2</sub> /0	S <sub>3</sub> /0			
S <sub>7</sub>	S <sub>8</sub> /0	S <sub>7</sub> /1	S <sub>4</sub> /1	S <sub>3</sub> /0			
S <sub>8</sub>	S <sub>8</sub> /0	S <sub>6</sub> /1	S <sub>5</sub> /1	S <sub>1</sub> /0			
	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	S <sub>4</sub>	S <sub>5</sub>	S <sub>6</sub>	S <sub>7</sub>
S <sub>2</sub>	X						
S <sub>3</sub>							
S <sub>4</sub>							
S <sub>5</sub>							
S <sub>6</sub>							
S <sub>7</sub>							
S <sub>8</sub>							

S/I	I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	I <sub>4</sub>			
S <sub>1</sub>	S <sub>1</sub> /0	S <sub>2</sub> /1	S <sub>5</sub> /1	S <sub>7</sub> /0			
S <sub>2</sub>	S <sub>2</sub> /1	S <sub>2</sub> /0	S <sub>6</sub> /0	S <sub>3</sub> /0			
S <sub>3</sub>	S <sub>3</sub> /1	S <sub>7</sub> /0	S <sub>4</sub> /0	S <sub>5</sub> /0			
S <sub>4</sub>	S <sub>1</sub> /0	S <sub>7</sub> /1	S <sub>4</sub> /1	S <sub>3</sub> /0			
S <sub>5</sub>	S <sub>5</sub> /0	S <sub>6</sub> /1	S <sub>5</sub> /1	S <sub>5</sub> /0			
S <sub>6</sub>	S <sub>2</sub> /1	S <sub>6</sub> /0	S <sub>2</sub> /0	S <sub>3</sub> /0			
S <sub>7</sub>	S <sub>8</sub> /0	S <sub>7</sub> /1	S <sub>4</sub> /1	S <sub>3</sub> /0			
S <sub>8</sub>	S <sub>8</sub> /0	S <sub>6</sub> /1	S <sub>5</sub> /1	S <sub>1</sub> /0			
S/I	S <sub>1</sub>	S <sub>2</sub>	S <sub>3</sub>	S <sub>4</sub>	S <sub>5</sub>	S <sub>6</sub>	S <sub>7</sub>
S <sub>2</sub>	X						
S <sub>3</sub>	X						
S <sub>4</sub>	(2,7)-(4,5)-(1,3)						
S <sub>5</sub>							
S <sub>6</sub>							
S <sub>7</sub>							
S <sub>8</sub>							

$S/I$	$I_1$	$I_2$	$I_3$	$I_4$	$I_5$
$S_1$	$S_1/0$	$S_2/1$	$S_3/1$	$S_6/1$	$S_1/0$
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$	
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_3/0$	
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$	
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$	
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_3/0$	
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$	
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$	
	$S_1$	$S_2$	$S_3$	$S_4$	$S_5$
$S_2$	X				
$S_3$	X				
$S_4$	X				
$S_5$	(2,6)				
$S_6$					
$S_7$					
$S_8$					

$S/I$	$I_1$	$I_2$	$I_3$	$I_4$			
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$			
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$			
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_3/0$			
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$			
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_3/0$			
$S_7$	$S_6/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$			
	$S_1$	$S_2$	$S_3$	$S_4$	$S_5$	$S_6$	$S_7$
$S_2$	X						
$S_3$	X	(2,7)(4,6)					
$S_4$	X	X					
$S_5$	(2,6)	X					
$S_6$	X	o					
$S_7$	(2,7)(4,5)						
	(2,6)						

$S/I$	$I_1$	$I_2$	$I_3$	$I_4$			
$S_1$	$S_1/0$	$S_2/1$	$S_3/1$	$S_1/0$			
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$			
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_3/0$			
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$			
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_3/0$			
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$			
	$S_1$	$S_2$	$S_3$	$S_4$	$S_5$	$S_6$	$S_7$
$S_2$	X						
$S_3$	X	(2,7)(4,6)					
$S_4$	X	X					
$S_5$	(2,6)◦	X					
$S_6$	X	◦					
$S_7$	(2,7)(4,5)						
$S_8$	(2,6)◦						

$S/I$	$I_1$	$I_2$	$I_3$	$I_4$			
$S_1$	$S_1/0$	$S_2/1$	$S_3/1$	$S_1/0$			
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$			
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_3/0$			
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$			
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_3/0$			
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$			
$S_1$	$S_1$	$S_2$	$S_3$	$S_4$	$S_5$	$S_6$	$S_7$
$S_2$	X						
$S_3$	X		(2,7)(4,6)X				
$S_4$	X	X					
$S_5$	(2,6) $\circ$	X					
$S_6$	X	$\circ$					
$S_7$	(2,7)(4,5)X	X					
$S_8$	(2,6) $\circ$						

$S/I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$
$S_3$	$S_3/1$	$S_5/0$	$S_4/0$	$S_5/0$
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$
$S_6$	$S_2/1$	$S_2/0$	$S_5/0$	$S_5/0$
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$
	$S_1$	$S_2$	$S_3$	
$S_2$	X			
$S_3$	X	X		
$S_4$	X		X	
$S_5$	$(2,6) \circ$	X	X	
$S_6$	X	$\circ$	$(2,3)(6,7)(2,4)$	
$S_7$	X	X		
$S_8$	$(2,6) \circ$	X		

$S//I$	$I_1$	$I_2$	$I_3$	$I_4$			
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$			
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$			
$S_3$	$S_3/1$	$S_5/0$	$S_4/0$	$S_5/0$			
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$			
$S_6$	$S_2/1$	$S_2/0$	$S_5/0$	$S_5/0$			
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$			
	$S_1$	$S_2$	$S_3$	$S_4$	$S_5$	$S_6$	$S_7$
$S_2$	X						
$S_3$	X	X					
$S_4$	X	X	X				
$S_5$	(2,6) $\circ$	X	X	(1,5)(6,7)(3,5)			
$S_6$	X	$\circ$	X				
$S_7$	X	X	X				
$S_8$	(2,6) $\circ$	X	X				

$S//I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_5/0$
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$
$S_6$	$S_2/1$	$S_2/0$	$S_5/0$	$S_5/0$
$S_7$	$S_8/0$	$S_7/1$	$S_5/1$	$S_3/0$
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$
	$S_1$	$S_2$	$S_3$	$S_4$
$S_1$	X			
$S_2$	X	X		
$S_3$	X	X		
$S_4$	X	X	X	
$S_5$	$(2,6) \circ$	X	X	X
$S_6$	X	$\circ$	X	X
$S_7$	X	X	X	$(1,8) \circ$
$S_8$	$(2,6) \circ$	X	X	

$S/I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_5/0$
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$
$S_6$	$S_2/1$	$S_2/0$	$S_5/0$	$S_5/0$
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$
	$S_1$	$S_2$	$S_3$	$S_4$
$S_1$	X			
$S_2$	X	X		
$S_3$	X	X		
$S_4$	X	X	X	
$S_5$	(2,6) $\circ$	X	X	X
$S_6$	X	$\circ$	X	X
$S_7$	X	X	X	(1,8) $\circ$
$S_8$	(2,6) $\circ$	X	X	(1,8)(7,6)(4,5)

$S//I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_5/0$
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$
$S_6$	$S_2/1$	$S_2/0$	$S_5/0$	$S_5/0$
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$
	$S_1$	$S_2$	$S_3$	$S_4$
$S_2$	X			
$S_3$	X	X		
$S_4$	X	X	X	
$S_5$	$(2,6)^\circ$	X	X	X
$S_6$	X	$\circ$	X	X
$S_7$	X	X	X	$(1,8)^\circ$
$S_8$	$(2,6)^\circ$	X	X	X



$S//I$	$I_1$	$I_2$	$I_3$	$I_4$			
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$			
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$			
$S_3$	$S_3/1$	$S_5/0$	$S_4/0$	$S_5/0$			
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$			
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$			
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_5/0$			
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_5/0$			
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$			
	$S_1$	$S_2$	$S_3$	$S_4$	$S_5$	$S_6$	$S_7$
$S_2$	X						
$S_3$	X	X					
$S_4$	X	X	X				
$S_5$	(2,6)◦	X	X	X			
$S_6$	X	◦	X	X	X		
$S_7$	X	X	X	(1,8)◦	X		
$S_8$	(2,6)◦	X	X	X	(1,5)◦		



$S \backslash I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_1/0$
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_3/0$
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_5/0$
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$

$S \backslash I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	X			
$S_2$	X	X		
$S_3$	X	X	X	
$S_4$	X	X	X	
$S_5$	(2,6) ◦	X	X	X
$S_6$	X	◦	X	X
$S_7$	X	X	X	(1,8) ◦
$S_8$	(2,6) ◦	X	X	(1,5) ◦

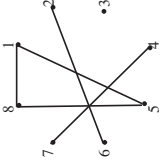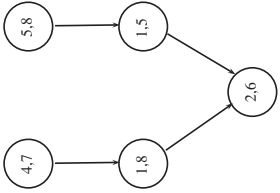We can sketch an undirected dependency graph using directed dependencies and find the connected components inside the graph. We can combine these cliques and discover equivalent states.



## State compatibility


A machine can sometimes be defined *incompletely*, either willingly or by the lack of information. An incomplete FSM transitions under some inputs lead to unspecified states or unspecified outputs. In order to eliminate the redundant states in such machines the concept of *compatibility relation* can be used.

### Compatibility Relation

A given binary relation  $\gamma$  on a set  $S$  is said to be a compatibility relation if and only if it is reflexive, symmetric and non-transitive. For example let function  $d(x, y)$  denote the distance between points  $x$  and  $y$ . If we define a relation  $R_\gamma = \{(a, b) | d(a, b) \leq 2, a, b \in \mathbb{N}\}$ . For this relation  $1\gamma 3$  and  $3\gamma 5$  holds but  $1\gamma 5$  doesn't. On the other hand transitive pairs can also be found like  $1\gamma 2$  and  $2\gamma 3$ .  $\gamma$  is a compatibility relation.


In the dependency table below we can see that some equivalencies depend on others. We can sketch a directed graph based on those dependencies.

	$S_1$	$S_2$	$S_3$	$S_4$	$S_5$	$S_6$	$S_7$
$S_2$	X						
$S_3$	X	X					
$S_4$	X	X	X				
$S_5$	(2,6) ◦	X	X	X			
$S_6$	X	◦	X	X	X		
$S_7$	X	X	X	(1,8) ◦	X	X	
$S_8$	(2,6) ◦	X	X	X	(1,5) ◦	X	X

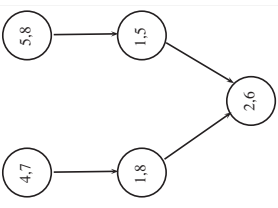

$S \backslash I$	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	$S_1/0$	$S_2/1$	$S_5/1$	$S_1/0$
$S_2$	$S_2/1$	$S_2/0$	$S_6/0$	$S_3/0$
$S_3$	$S_3/1$	$S_7/0$	$S_4/0$	$S_3/0$
$S_4$	$S_1/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_5$	$S_5/0$	$S_6/1$	$S_5/1$	$S_5/0$
$S_6$	$S_2/1$	$S_6/0$	$S_2/0$	$S_5/0$
$S_7$	$S_8/0$	$S_7/1$	$S_4/1$	$S_3/0$
$S_8$	$S_8/0$	$S_6/1$	$S_5/1$	$S_1/0$

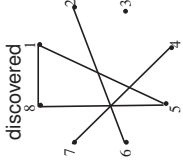If we rebuild our state table using the equivalence classes we have just discovered



	$I_1$	$I_2$	$I_3$	$I_4$
$S'_1$	$(S_1, S_5, S_8)$	$S'_1/0$	$S'_2/1$	$S'_1/1$
$S'_2$	$(S_2, S_6)$	$S'_2/1$	$S'_2/0$	$S'_2/0$
$S'_3$	$(S_3)$	$S'_3/1$	$S'_4/0$	$S'_3/0$
$S'_4$	$(S_4, S_7)$	$S'_1/0$	$S'_4/1$	$S'_3/0$

## Compatibility Class

A compatibility relation forms the compatibility classes over the set it has been defined. Each compatibility class is transitive inside. Differing from equivalence classes, compatibility classes may not be distinct.

### Maximal Compatibility Class

A compatible class is said to be maximal if it is not covered by any other compatible class. Class' graph is not a subgraph of another compatibility class.

For the following three compatibility classes  $(a, b, c, d) \supseteq (a, b, c) \supseteq (a, b)$ ,  $(a, b, c, d)$  is the maximal compatibility class.

**Cover**

A set of compatible classes covers machine  $\mathbb{M}$  if it contains all the states of the machine.

**Complete Cover**


The set of all the maximal compatible classes that covers machine  $\mathbb{M}$ .

**Example**

For the relation  $\gamma$  defined as

$$R_\gamma = \{a\gamma b, a\gamma c, a\gamma d, b\gamma c, b\gamma d, c\gamma d, b\gamma e, e\gamma f, e\gamma g, g\gamma f, g\gamma h\}$$

Let's sketch the relation graph.

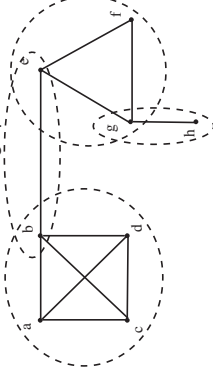

The complete cover of the graph is:  $\{\{a, b, c, d\}, \{b, e\}, \{e, f, g\}, \{g, h\}\}$ .  
For this example one can find a cover that doesn't contain  $\{b, e\}$  however the complete cover should contain  $\{b, e\}$  too.

**Compatibility of States**

States  $s_i$  and  $s_j$  are compatible, if and only if, for every possible input sequence applicable to them, the same output sequence is produced.  
Compatible states are denoted as  $s_i/s_j$ .

Let's consider the three states below

$$s_1 = ab\emptyset ef$$

$$s_2 = a\emptyset jef$$

$$s_3 = acfef$$

There exists two compatible classes  $s_1, s_2$  and  $s_2, s_3$  in this example.

State reduction using a complete cover may yield to a non-optimal result. In order to achieve optimal state reduction minimal closed covers should be used.

**Implied Compatible**

Under input  $i$ , a set of states  $S$  implies another set of states  $R$ , if  $R$  is a set of next states for  $S$ . If  $S$  is a compatible, then  $R$  is called an implied compatible of  $S$  under input  $i$ .

**Closed Cover**

A set of compatibles is closed if for every compatible contained in the set, all its implied compatibles are also contained in the same set.

**State Compatibility Conditions**

The necessary and sufficient conditions for two states in a state table to be compatible are: For all the inputs of those states

- Outputs should be the compatible
- Successing conditions should
  - be explicitly or implicitly compatible
  - not have any outputs that doesn't conform compatibility

State reduction using a complete cover may yield to a non-optimal result. In order to achieve optimal state reduction minimal closed covers should be used.

**Minimal Closed Cover**

A set of  $k$  compatibles forming the set  $\mathbb{S}$  is called a minimal closed cover: if and only if  $\mathbb{S}$  satisfies

- 1 Covering condition:  $\mathbb{S}$  covers the machine  $\mathbb{M}$
- 2 Closure condition:  $\mathbb{S}$  is closed
- 3 Minimal condition: A set of  $k - 1$  or less compatibles does not satisfy both covering condition and closure condition.

## Example

Let's consider the following incomplete state table:


	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	-	-	$S_5/1$	-
$S_2$	-	$S_5/1$	$S_4/-$	-
$S_3$	$S_3/0$	$S_2/1$	-	$S_1/0$
$S_4$	$S_3/0$	$S_1/1$	$S_4/0$	-
$S_5$	$S_4/0$	$-/1$	$S_3/-$	$S_4/-$

and its corresponding dependency table

	$S_1$	$S_2$	$S_3$	$S_4$
$S_2$	$S_4 - S_5$			
$S_3$	$\circ$	$S_2 - S_5$		
$S_4$	X	$S_1 - S_5$ X	$S_1 - S_2$	
$S_5$	$S_3 - S_5$ X	$S_3 - S_4$	$S_3 - S_4, S_1 - S_4$ X	$S_3 - S_4$
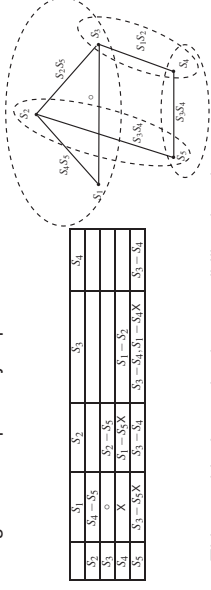
## Example


Let's build the relation graph of the state compatibilities. We label edges as compatibility dependencies.



This machine's maximal compatibility class is  $\{(S_1, S_2, S_3), (S_3, S_4), (S_2, S_5), (S_4, S_5)\}$
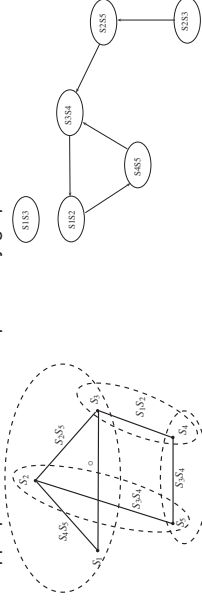
## Example

The relation graph points out a four state machine, it may be appropriate to examine dependency graph of the relation as well.



For the graph above,  $(S_1, S_2)$ ,  $(S_3, S_4)$  and  $(S_4, S_5)$  forms a compatibility class having closure property and covering all the states of the system.

## Example

At the end of the process we can build a new state table for the machine.

	$I_1$	$I_2$	$I_3$	$I_4$
$S_1$	-	-	$S_5/1$	-
$S_2$	-	$S_5/1$	$S_4/-$	-
$S_3$	$S_3/0$	$S_2/1$	-	$S_1/0$
$S_4$	$S_3/0$	$S_1/1$	$S_4/0$	-
$S_5$	$S_4/0$	$-/1$	$S_3/-$	$S_4/-$

A Mealy model reduced machine

	$I_1$	$I_2$	$I_3$	$I_4$
$(S_1, S_2)$	a	-	c/1	-
$(S_3, S_4)$	b	b/0	a/1	b/c/0
$(S_1, S_5)$	-	b/0	a/1	b/0

A Moore model machine

	$I_1$	$I_2$	$I_3$	$I_4$	O
u	a/1	-	z	z	-
v	a/0	-	z	z	-
w	b/0	w	u	w	v
z	c/1	w	u	w	1